

Hans-Joachim Adam / Mathias Adam

SPS

Programmieren in Anweisungsliste nach IEC
61131-3 (Lösungsbuch)

1. August 2012

adamis

Vorwort

In diesem Buch erhalten Sie Lösungsvorschläge zu den Übungen des zugehörigen Lehrbuchs. Sie können dieses Lösungsbuch von der Webseite der Autoren¹ herunterladen.

Für die meisten Übungen sind Musterlösungen verfügbar: Jede Übung hat einen eindeutigen Namen, unter dem die Lösung zu finden ist.

Die Übungen zum Teil I, Kapitel 2 bis 4, Digitaltechnik, können mit dem „Digital-Simulator“ durchgeführt werden. Dieses Programm kann kostenlos aus dem Internet heruntergeladen werden.²

Die Lösungsvorschläge für die Übungen zum Teil II, SPS-Technik, sind für das SPS-Simulationsprogramm „PLC-lite“, welches Sie von der Webseite der Autoren herunterladen können. Dort werden auch direkt in „PLC-lite“ einsetzbare Lösungsvorschläge für die Übungen und laufend Updates und Ergänzungen zu „PLC-lite“ bereitgestellt.

Bühl, Juni 2012

*Hans-Joachim Adam
Mathias Adam*

¹ <http://www.adamis.de/sps/>

² <http://sourceforge.net/projects/digisimulator/files/>

Inhaltsverzeichnis

Teil I Digitaltechnik

1	Grundlagen: Zahlensysteme, Dualzahlen und Codes	3
2	Logische Funktionen und Boolesche Algebra	7
3	Speicherglieder	15
4	Dynamische Speicherglieder und Zähler	21

Teil II SPS-Technik

5	Schaltnetze mit SPS	29
6	Schaltungen mit Signalspeichern	37
7	Zeitfunktionen mit SPS	47
8	Zähler mit SPS	59
9	Funktionsbausteine	75
10	Sprünge, Schleifen und Wiederholungen	83
11	Funktionen	93
12	Ablaufsteuerungen	107
13	Wiederholungsaufgaben	117
	Sachverzeichnis	141

Teil I
Digitaltechnik

Im ersten Teil des Buches behandeln wir die Digitaltechnik. Dieser Abschnitt dient als Vorbereitung zur SPS-Programmierung, die im Teil II behandelt wird.

Kapitel 1

Grundlagen: Zahlensysteme, Dualzahlen und Codes

Übung 1.1 Zahlenwörter

	deutsch	english	français	espagnol	italiano
0	Null	Zero	zéro	cero	zero
1	eins	one	un	uno	uno
2	zwei	two	deux	dos	due
3	drei	three	trois	tres	tre
4	vier	four	quatre	cuatro	quattro
5	fünf	five	cinq	cinco	cinque
6	sechs	six	six	seis	sei
7	sieben	seven	sept	siete	sette
8	acht	eight	huit	ocho	otto
9	neun	nine	neuf	nueve	nove
10	zehn	ten	dix	diez	dieci
11	elf	eleven	onze	once	undici
12	zwölf	twelve	douze	doce	dodici
13	dreizehn	thirteen	treize	trece	trédici
14	vierzehn	fourteen	quatorze	catorce	quattordici
15	fünfzehn	fifteen	quinze	quince	quindici
16	sechzehn	sixteen	seize	dieciséis	sedici
17	siebzehn	seventeen	dix-sept	diecisiete	diciasette
18	achtzehn	eighteen	dix-huit	dieciocho	diciotto
19	neunzehn	nineteen	dix-neuf	diecinueve	dicianove
20	zwanzig	twenty	vingt	veinte	venti

Übung 1.2 Lösung siehe Abb. 1.1

Abb. 1.1 Bündelfelder zu den Übungen 1.2 und 1.3

	100	10	1
②	①	①	
1	4	4	

Übung 1.3 Lösung siehe Abb. 1.1**Übung 1.4** Ergebnisse:

a) 412 b) 130413

Übung 1.5

	32	16	8	4	2	1
⑤	④	③	②	①	①	
	N	N	N	N		N
1	0	1	0	1	1	

Abb. 1.2 Zweierbündelung zu Übung 1.5**Übung 1.6** Ergebnisse:

- a. $011 = 3$ b. $10101010 = 170$ c. $111 = 7$
d. $10010010 = 146$ e. $100 = 4$ f. $01010101 = 85$
g. $10000 = 16$ h. $10100 = 20$ i. $110 = 6$
j. $10000000 = 128$ k. $1111 = 15$ l. $10000101 = 133$

Übung 1.7 Ergebnisse:

- a. $3 = 11$ b. $9 = 1001$ c. $15 = 1111$
d. $20 = 10100$ e. $31 = 11111$ f. $45 = 101101$
g. $99 = 1100011$ h. $189 = 10111101$ i. $200 = 11001000$
j. $266 = 100001010$ k. $278 = 100010110$ l. $311 = 100110111$
m. $499 = 111110011$ n. $556 = 100001110$

Kapitel 2

Logische Funktionen und Boolesche Algebra

Übung 2.1 (EQUAL21) ¹

 


Abb. 2.1 Lösung zu Übung 2.1

Übung 2.2 (AND21)

Keine Musterlösung.

Übung 2.3 (HEAT21)

 


Abb. 2.2 Lösung zu Übung 2.3

¹ Mit dem „Digitalsimulator“ (<http://www.draw2d.org/digitalsimulator/about>) wurden Musterlösungen erarbeitet, die Sie von der Webseite der Autoren herunterladen können.

Übung 2.4 (MIXER21)

Keine Musterlösung.

 
Übung 2.5 (ALARM21)

Abb. 2.3 Lösung zu Übung 2.5

Übung 2.6 (FLASH21)

a	G	X
0	0	0
0	1	0
1	0	0
1	1	1

 
 


Abb. 2.4 Lösung zu Übung 2.6

Übung 2.7 (FLASH22)

Lösung siehe Abb. 2.5.

Übung 2.8 (NAND21)

Keine Musterlösung.

Übung 2.9 (NOR21)

Keine Musterlösung.

Übung 2.10 (LOGIK21)


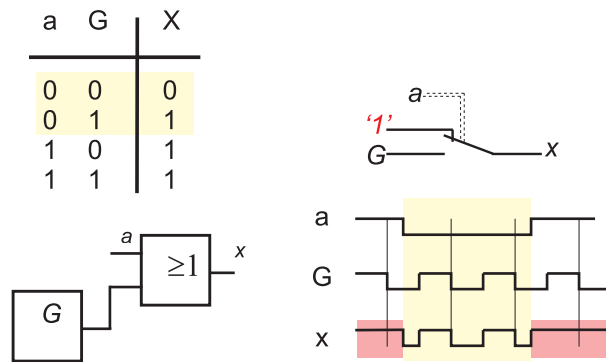


Abb. 2.5 Lösung zu Übung 2.7


Funktionstabellen, Logikpläne und Funktionsgleichungen zu Übung 2.10:

Funktion 1	Funktion 2																														
<table border="1" style="display: inline-table; margin-right: 20px;"> <thead> <tr> <th>a</th> <th>b</th> <th>x</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table> <p>$x = a \wedge b$</p>	a	b	x	0	0	0	1	0	0	0	1	0	1	1	1	<table border="1" style="display: inline-table; margin-right: 20px;"> <thead> <tr> <th>a</th> <th>b</th> <th>x</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table> <p>$x = a \wedge \bar{b}$</p>	a	b	x	0	0	0	1	0	1	0	1	0	1	1	0
a	b	x																													
0	0	0																													
1	0	0																													
0	1	0																													
1	1	1																													
a	b	x																													
0	0	0																													
1	0	1																													
0	1	0																													
1	1	0																													
<table border="1" style="display: inline-table; margin-right: 20px;"> <thead> <tr> <th>a</th> <th>b</th> <th>x</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table> <p>$x = \bar{a} \wedge b$</p>	a	b	x	0	0	0	1	0	0	0	1	1	1	1	0	<table border="1" style="display: inline-table; margin-right: 20px;"> <thead> <tr> <th>a</th> <th>b</th> <th>x</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table> <p>$x = \bar{a} \wedge \bar{b}$</p>	a	b	x	0	0	1	1	0	0	0	1	0	1	1	0
a	b	x																													
0	0	0																													
1	0	0																													
0	1	1																													
1	1	0																													
a	b	x																													
0	0	1																													
1	0	0																													
0	1	0																													
1	1	0																													
<table border="1" style="display: inline-table; margin-right: 20px;"> <thead> <tr> <th>a</th> <th>b</th> <th>x</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table> <p>$x = a \vee b$</p>	a	b	x	0	0	0	1	0	1	0	1	1	1	1	1	<table border="1" style="display: inline-table; margin-right: 20px;"> <thead> <tr> <th>a</th> <th>b</th> <th>x</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table> <p>$x = \bar{a} \vee b$</p>	a	b	x	0	0	1	1	0	0	0	1	1	1	1	1
a	b	x																													
0	0	0																													
1	0	1																													
0	1	1																													
1	1	1																													
a	b	x																													
0	0	1																													
1	0	0																													
0	1	1																													
1	1	1																													

Funktion 7			Funktion 8		
a	b	x	a	b	x
0	0	1	0	0	1
1	0	1	1	0	1
0	1	0	0	1	1
1	1	1	1	1	0

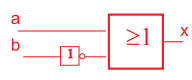

$x = a \vee \bar{b}$

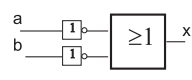

$x = \bar{a} \vee \bar{b}$


Übung 2.11 (LOGIK22)

Keine Musterlösung.

Übung 2.12 (LOGIK23)

Funktion 9 zu Übung 2.12


a	b	x	x ₁	x ₂
0	0	0	0	0
1	0	0	0	0
0	1	1	1	0
1	1	1	0	1

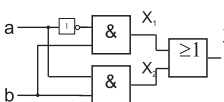

$X = (\bar{a} \wedge b) \vee (a \wedge b)$

Funktion 10 zu Übung 2.12


a	b	x	x ₁	x ₂
0	0	1	1	0
1	0	1	0	1
0	1	0	0	0
1	1	0	0	0

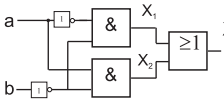

$X = (\bar{a} \wedge \bar{b}) \vee (a \wedge b)$

Funktion 11 zu Übung 2.12


a	b	x	x ₁	x ₂
0	0	0	0	0
1	0	1	1	0
0	1	1	0	1
1	1	0	0	0

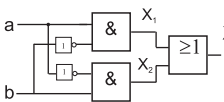

$X = (a \wedge \bar{b}) \vee (\bar{a} \wedge b)$

Funktion 12 zu Übung 2.12


a	b	x	x ₁	x ₂
0	0	1	1	0
1	0	0	0	0
0	1	0	0	0
1	1	1	0	1

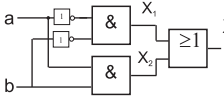

$X = (\bar{a} \wedge \bar{b}) \vee (a \wedge b)$

Funktion 13 zu Übung 2.12


a	b	x	x ₁	x ₂
0	0	1	1	0
1	0	0	0	0
0	1	1	0	1
1	1	0	0	0

 

$$X = (\bar{a} \wedge \bar{b}) \vee (\bar{a} \wedge b)$$

Funktion 14 zu Übung 2.12

a	b	x	x ₁	x ₂
0	0	0	0	0
1	0	1	1	0
0	1	0	0	0
1	1	1	0	1

 

$$X = (a \wedge \bar{b}) \vee (a \wedge b)$$

Übung 2.13 (SWITCH21)

a	b	Y
0	0	0
1	0	1
0	1	1
1	1	0

Abb. 2.6 Lösung zu Übung 2.13

Übung 2.14 (MINTERM21)

E ₃	E ₂	E ₁	X ₁	X ₂	X
0	0	0	0	0	0
1	0	0	0	0	0
0	1	0	0	0	0
1	1	0	0	0	0
0	0	1	0	0	0
1	0	1	0	0	0
0	1	1	0	1	1
1	1	1	1	0	1

$$X = (E_1 \wedge E_2 \wedge E_3) \vee (\bar{E}_1 \wedge E_2 \wedge E_3)$$

Abb. 2.7 Lösung zu Übung 2.14

Übung 2.15 (SWITCH22)

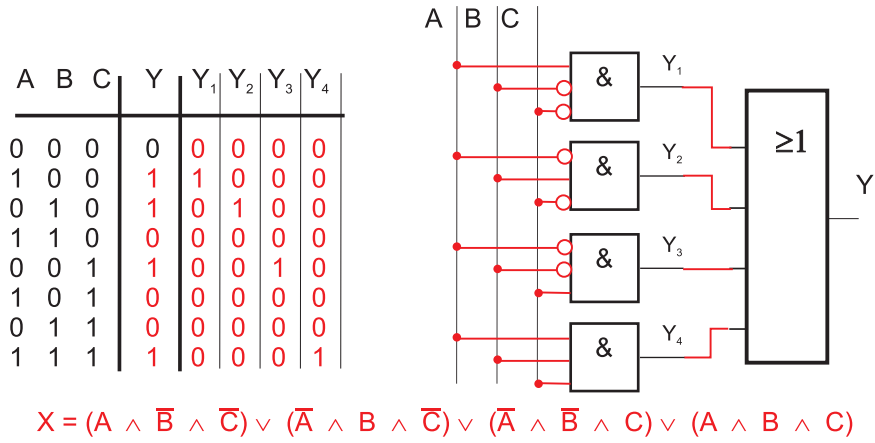


Abb. 2.8 Lösung zu Übung 2.15

Übung 2.16 (ALARM22)

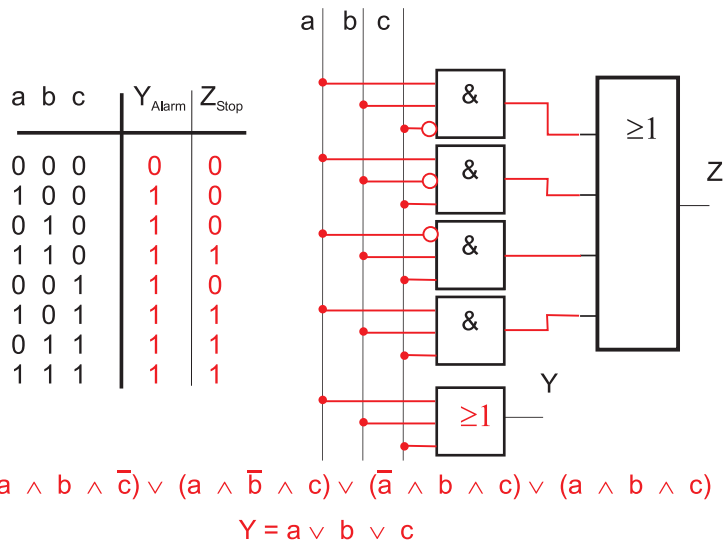


Abb. 2.9 Lösung zu Übung 2.16

Übung 2.17 (LOGIK24)

a	b	c	Y_1	$a \wedge b$	$a \wedge c$	$b \wedge c$	Y_2
0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0
1	1	0	1	1	0	0	1
0	0	1	0	0	0	0	0
1	0	1	1	0	1	0	1
0	1	1	1	0	0	1	1
1	1	1	1	1	1	1	1

Abb. 2.10 Lösung zu
Übung 2.17

Übung 2.18 (LOGIK25)

a	b	$\bar{a} \wedge b$	$a \wedge \bar{b}$	X	$a \vee b$	$\bar{a} \vee \bar{b}$	Y
0	0	0	0	0	0	1	0
0	1	1	0	1	1	1	1
1	0	0	1	1	1	1	1
1	1	0	0	0	1	0	0

Abb. 2.11 Lösung zu Übung 2.18

Übung 2.19 (LOGIK26)

Lösung siehe Abb. 2.12.

S	R	Ya	$\overline{R} \wedge Ya$	Y	$\overline{R \vee \overline{Ya}}$
0	0	0	0	0	0
1	0	0	0	1	0
0	1	0	0	0	0
1	1	0	0	1	0
0	0	1	1	1	1
1	0	1	1	1	1
0	1	1	0	0	0
1	1	1	0	1	0

Abb. 2.12 Lösung zu
Übung 2.19

Kapitel 3

Speicherglieder

Übung 3.1 (RSFF31)
Keine Musterlösung.


Übung 3.2 (ALARM31)

Abb. 3.1 Alarmschaltung I
zu Übung 3.2



Übung 3.3 (RSFF32)
Keine Musterlösung.


Übung 3.4 (RSFF33)

 

a	b	Y
0	0	Y
1	0	1 (Setzen)
0	1	0 (Rücksetzen)
1	1	0 (Priorität)

Abb. 3.2 Lösung zu Übung 3.4

Abb. 3.3 Lösung zu Übung 3.5

 

Übung 3.5 (RSFF34)

Lösung siehe Abb. 3.3

Übung 3.6 (LIFT31)

Lösung siehe Abb. 3.4

 


Abb. 3.4 Lösung zu Übung 3.6

Setzbedingungen für Rechtslauf:

AUF und nicht Linkslauf

Setzbedingungen für Linkslauf:

AB und nicht Rechtslauf

Rücksetzbedingungen:

AUS

Aktionen:

FF "Rechtslauf" gesetzt -> Motor aufwärts

FF "Linkslauf" gesetzt -> Motor abwärts

Übung 3.7 (LIFT32)

Lösung siehe Abb. 3.5

Übung 3.8 (LIFT33)

Lösung siehe Abb. 3.6

Übung 3.9 (RSFF35)

Lösung siehe Abb. 3.7

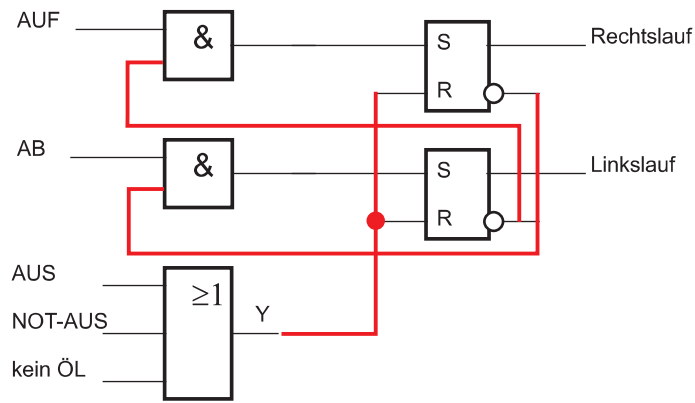


Abb. 3.5 Lösung zu Übung 3.7

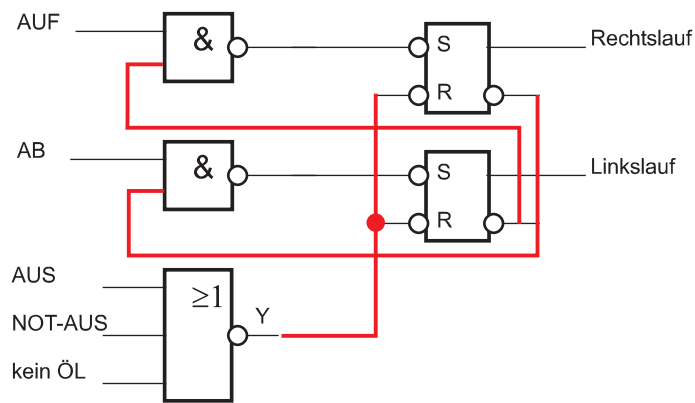


Abb. 3.6 Lösung zu Übung 3.8

 


Abb. 3.7 Lösung zu Übung 3.9

 


Abb. 3.8 Lösung zu Übung 3.10

Übung 3.10 (RSFF36)

Lösung siehe Abb. 3.8

 
Übung 3.11 (RSFF37)

Abb. 3.9 Lösung zu Übung 3.11

Übung 3.12 (RSFF38)

Lösung siehe Abb. 3.10

 


Abb. 3.10 Lösung zu Übung 3.12

Übung 3.13 (RSFF39)

Lösung siehe Abb. 3.11

 


Abb. 3.11 Lösung zu Übung 3.13

Übung 3.14 (ALARM32)

Lösung siehe Abb. 3.12

 


Abb. 3.12 Lösung zu Übung 3.14

Übung 3.15 (TANK31)

Lösung siehe Abb. 3.13

 


Abb. 3.13 Lösung zu Übung 3.15

Übung 3.16 (TANK32)

Lösung siehe Abb. 3.14

 
 


Abb. 3.14 Lösung zu Übung 3.16

Übung 3.17 (ALARM33)

Lösung siehe Abb. 3.15

**Abb. 3.15** Lösung zu Übung 3.17

Kapitel 4

Dynamische Speicherglieder und Zähler

Übung 4.1 (RSFF41)

Lösung siehe Abb. 4.1.

 


Abb. 4.1 Lösung zu Übung 4.1

Übung 4.2 (RSFF42)

Keine Musterlösung.

Übung 4.3 (RSFF43)

Lösung siehe Abb. 4.2

 


Abb. 4.2 Lösung zu Übung 4.3

Übung 4.4 (JKFF41)

Lösung siehe Abb. 4.3

 


Abb. 4.3 Lösung zu Übung 4.4

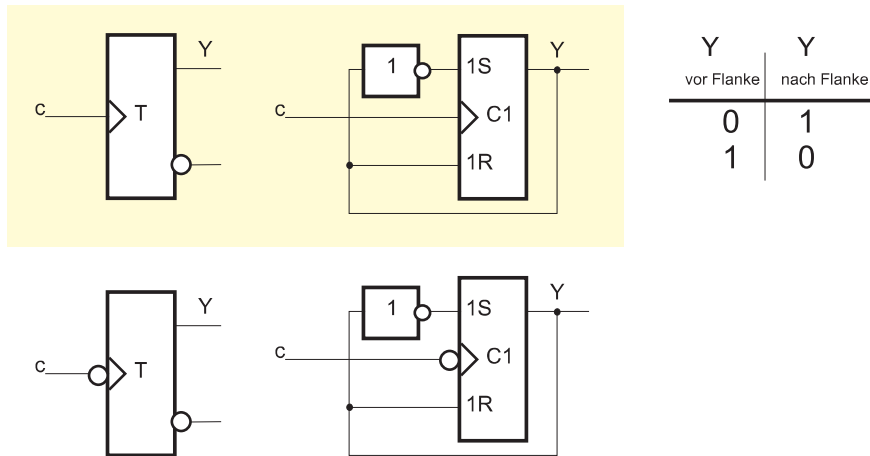


Abb. 4.4 Lösung zu Übung 4.5

Übung 4.5 (TFF41)

Lösung siehe Abb. 4.4

Übung 4.6 (TANK41)

Lösung siehe Abb. 4.5

Wird an Stelle des T-Flip-Flop ein „gewöhnliches“ RS-Flip-Flop verwendet, dann sind zwei getrennte Taster für 'Start' und 'Stopp' oder ein Taster mit Umschaltkontakt erforderlich. Mit dem T-Flip-Flop genügt ein einfacher Taster und ein einfacher Tastendruck.

Übung 4.7 (COUNT41)

Siehe auch Abb. 4.6.

Die negative Flanke bringt das erste FlipFlop zum kippen, der Ausgang 2^0 wird zu '0'. Dadurch entsteht eine negative Flanke, die das zweite FlipFlop kippt. Dies geschieht aber erst mit einer zeitlichen Verzögerung. Die Folge: kurzzeitig erscheint

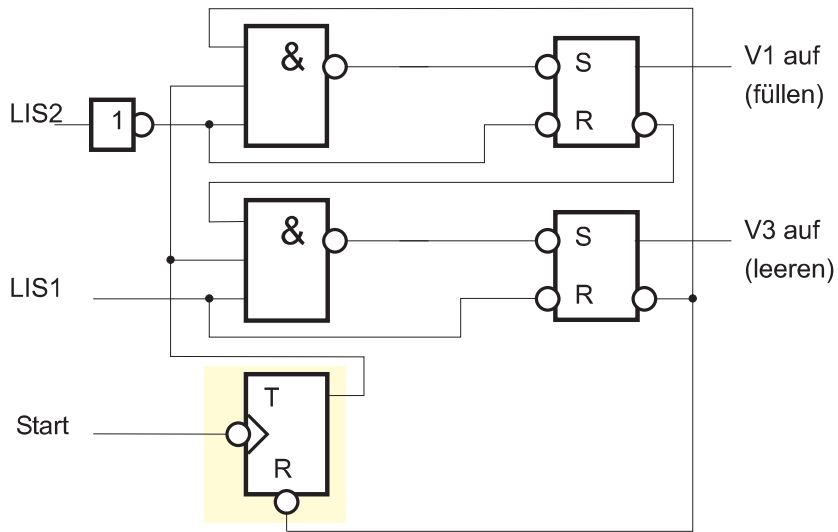


Abb. 4.5 Schaltung zu Übung 4.6

die falsche Zahl 1110. Das Kippen setzt sich fort, so dass nacheinander die weiteren falschen Zahlen 1100 und 1000 erscheinen bis erst zum Schluss sich das richtige Ergebnis 0000 einstellt.

Dez =	HEX	=	8	4	2	1
...						
14	E		1	1	1	0
15	F		1	1	1	1
0	0		0	0	0	0
1	1		0	0	0	1
...						

 


Abb. 4.6 Lösung zu Übung 4.7

Übung 4.8 (COUNT42)

Keine Musterlösung.

Übung 4.9 (COUNT43)

Lösung siehe Abb. 4.7.

 


Abb. 4.7 Zeitdiagramm für 4-bit Zähler

Übung 4.10 (COUNT44)

Lösung siehe Abb. 4.8.

 


Abb. 4.8 Lösung zu Übung 4.10

Übung 4.11 (COUNT45)

Lösung siehe Abb. 4.9.

Übung 4.12 (COUNT46)

Lösung siehe Abb. 4.10

Übung 4.13 (COUNT47)

Lösung siehe Abb. 4.11

 


Abb. 4.9 Lösung zu Übung 4.11

 


Abb. 4.10 Lösung zu Übung 4.12

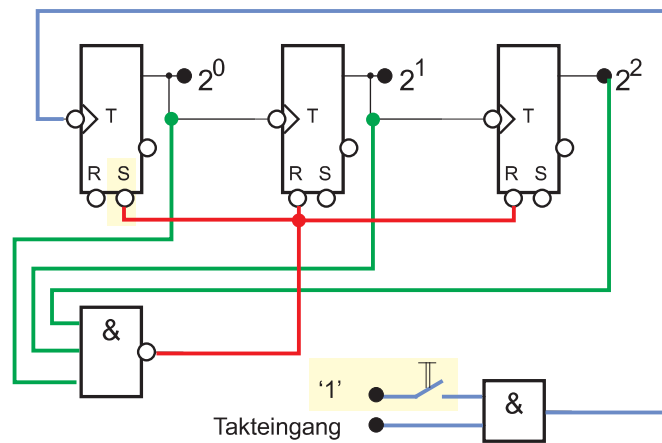


Abb. 4.11 Lösung zu Übung 4.13

Teil II
SPS-Technik

Im zweiten Teil des Buches behandeln wir die SPS-Technik.

Kapitel 5

Schaltnetze mit SPS

Auf der Webseite¹ der Autoren zu diesem Buch steht das Programm PLC-lite zur Verfügung, mit dessen Hilfe Sie alle Übungen durchführen können.

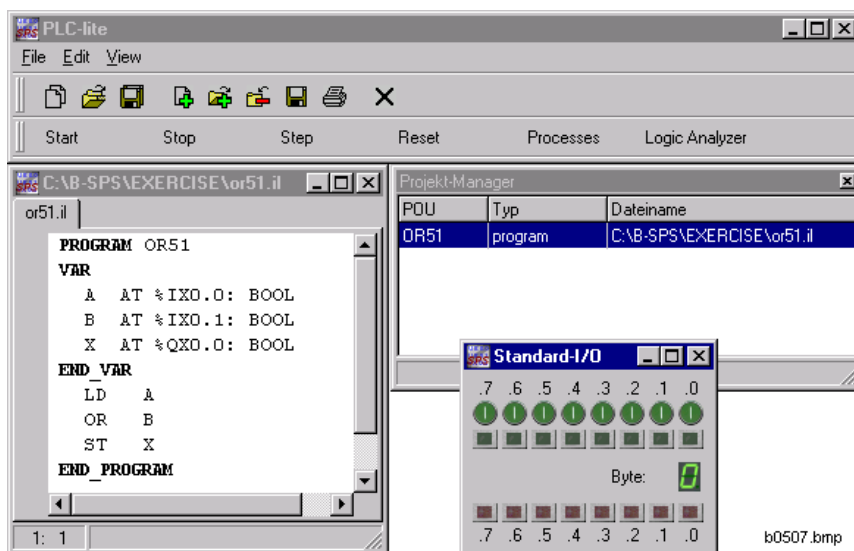


Abb. 5.1 PLC-lite: Hauptfenster, Editorfenster und Projektmanager

Nach dem Start des Programmes öffnen sich zunächst drei Fenster: das Hauptfenster mit den Bedienelementen zum Steuern des Projektes und der simulierten SPS, sowie das Editorfenster mit dem Editor, in dem Sie die Anweisungsliste eintippen können und das Fenster mit dem Projektmanager.

Klicken Sie im Hauptfenster auf den Button „Visualization“ (bzw. „Processes“ in älteren Versionen von PLC-lite) und wählen Sie zunächst „Standard-I/O“ aus. Über

¹ <http://www.adamis.de/sps/>

dieses Menü können Sie in späteren Übungen die zugehörigen Anzeigeelemente und Prozessmodelle öffnen.

Zum Einstellen der Eingangswerte für die SPS klicken Sie mit der Maus auf die grünen Taster. Die unteren, roten „Leuchtdioden“ (LEDs) zeigen Ihnen den Ausgangswert. Eine „leuchtende“ LED bedeutet eine logische ‚1‘.

Die Eingänge wirken als Taster, wenn Sie mit der Maus klicken. Wenn Sie die Maus bei gedrückt gehaltener linker Maustaste von dem Taster wegziehen, bleibt er „eingerastet“. Der Eingang bleibt dann auf Dauer eingeschaltet, bis Sie wieder auf dem Eingang klicken. Somit haben Sie einen „Schalter“ am Eingang.

Übung 5.1 (OR51)

Verwenden in PLC-lite zur Visualisierung den Prozess „Standard I/O“. Klicken Sie in der oberen Reihe die „Taster“. Es leuchten die dem jeweiligen Eingang zugehörigen grünen LEDs auf, und in der unteren Reihe die dem Ausgang zugeordneten roten LEDs.

```
PROGRAM OR51
(*Processes: *)
(* Standard-I/O byte 0 *)
VAR
  a AT %IX0.0: BOOL
  b AT %IX0.1: BOOL
  x AT %QX0.0: BOOL
END_VAR
LD a
OR b
ST x
END_PROGRAM
```

Übung 5.2 (AND51)

Beachten Sie bei der Simulation mit PLC-lite, dass Sie die Taster „festklemmen“ können, indem Sie mit der Maus auf den Taster fahren, die linke Maustaste drücken, festhalten und dann herunter fahren. Der Taster bleibt dadurch gedrückt.

Eine nützliche Funktion ist der *Einzel schrittmodus*. Ein Klick auf ‚Step‘ führt in der Anweisungsliste den nächsten Befehl aus und wartet dann. Ein Klick auf ‚Cycle‘ arbeitet alle Anweisungen einmal durch und stoppt am Anfang der Anweisungsliste.

Diejenige Anweisung, welche beim nächsten Schritt ausgeführt werden wird, wird im Editor hervorgehoben dargestellt. Im sich gleichzeitig öffnenden Fenster ‚Watch expressions‘ werden Ihnen die aktuellen Werte der Variablen und des aktuellen Ergebnis (CR) angezeigt.

```
PROGRAM AND51
(*Processes: *)
(* Standard-I/O byte 0 *)
VAR
```

```

A   AT %IX0.0: BOOL
B   AT %IX0.1: BOOL
X   AT %QX0.0: BOOL
END_VAR
LD   A
AND  B
ST   X
END_PROGRAM

```

Übung 5.3 (MIXER51)

Zum Füllen bzw. Leeren des Kessels von Hand, bitte die Taster neben V3 bzw. V4 drücken.

```

PROGRAM MIXER51
(*Processes: *)
(* Boiler *)
VAR
MixerSwitch AT %IX0.0: BOOL
HeaterButton AT %IX0.7: BOOL
Mixer AT %QX0.6: BOOL
Heating AT %QX0.5: BOOL
V4 AT %QX0.4: BOOL
END_VAR
LD MixerSwitch
AND HeaterButton
STN V4
LD MixerSwitch
ST Mixer
LD HeaterButton
ST Heating
END_PROGRAM

```

Übung 5.4 (NAND51)

```

PROGRAM NAND51
(*Processes: *)
(* Standard-I/O byte 0 *)
VAR
A   AT %IX0.0: BOOL
B   AT %IX0.1: BOOL
X   AT %QX0.0: BOOL
Y   AT %QX0.1: BOOL
END_VAR
LD   A

```

```

AND B
STN X
LDN A
ORN B
ST Y
END_PROGRAM

```

Übung 5.5 (NOR51)

```

PROGRAM NOR51
(*Processes: *)
(* Standard-I/O byte 0 *)
VAR
  A AT %IX0.0: BOOL
  B AT %IX0.1: BOOL
  X AT %QX0.0: BOOL
  Y AT %QX0.1: BOOL
END_VAR
LD A
OR B
STN X
LDN A
ANDN B
ST Y
END_PROGRAM

```

Übung 5.6 (BOILER51)

```

PROGRAM Boiler51
(*Processes: *)
(* Boiler *)
VAR
  Sw1 AT %IX0.0: BOOL
  TIC AT %IX0.5: BOOL
  Heat AT %QX0.5: BOOL
END_VAR
LD Sw1
ANDN TIC
ST Heat
END_PROGRAM

```

Übung 5.7 (BOILER52)

```

PROGRAM Boiler52
(*Processes: *)

```

```

(* Boiler *)
VAR
  Sw1 AT %IX0.0: BOOL
  TIC AT %IX0.5: BOOL
  Heat AT %QX0.5: BOOL
  Start AT %IX0.7: BOOL
  Mixer AT %QX0.6: BOOL
END_VAR
LD Sw1
ANDN TIC
ST Heat
LD Start
ST Mixer
END_PROGRAM

```

Übung 5.8 (BOILER53)

Zum Füllen bzw. Leeren des Kessels von Hand, bitte die Taster neben V3 bzw. V4 drücken.

```

PROGRAM Boiler53
(*Processes: *)
(* Boiler *)
VAR
  Sw1 AT %IX0.0: BOOL
  TIC AT %IX0.5: BOOL
  Heat AT %QX0.5: BOOL
  Start AT %IX0.7: BOOL
  Mixer AT %QX0.6: BOOL
  LIS3 AT %IX0.3: BOOL
  Warn AT %QX0.7: BOOL
END_VAR
LD Sw1
ANDN TIC
ST Heat
LD Start
ST Mixer
LDN LIS3
AND Start
ST Warn
END_PROGRAM

```

Übung 5.9 (BOILER54)

```

PROGRAM Boiler54
(*Processes: *)

```

```

(* Boiler *)
VAR
  Sw1 AT %IX0.0: BOOL
  TIC AT %IX0.5: BOOL
  Heat AT %QX0.5: BOOL
  Start AT %IX0.7: BOOL
  Mixer AT %QX0.6: BOOL
  LIS3 AT %IX0.3: BOOL
  Warn AT %QX0.7: BOOL
  On_LED AT %QX0.0: BOOL
END_VAR
LD Sw1
ANDN TIC
ST Heat
LD Start
ST Mixer
LDN LIS3
AND Start
ST Warn
LD Heat
ST On_LED
END_PROGRAM

```

Übung 5.10 (POWER51)

```

PROGRAM POWER51a
(*Processes: *)
(* Standard-I/O byte 0 *)
VAR
  a AT %IX0.0: bool
  b AT %IX0.1: bool
  c AT %IX0.2: bool
  x AT %QX0.0: bool
  y AT %QX0.1: bool
END_VAR
LD a
OR b
ST x
LD x
AND c
ST y
END_PROGRAM

```

Weil das Aktuelle Ergebnis (CR) erhalten bleibt, ist die Zwischenspeicherung auf 'x' nicht erforderlich. Das können sie mittels des Einzelschrittmodus in PLC-lite nachvollziehen: wiederholt den Button "Step" klicken und im Fenster „Watch expressions“ die Wertezuweisungen verfolgen.


```

PROGRAM POWER51b
(*Processes: *)
(* Standard-I/O byte 0 *)
VAR
  a AT %IX0.0: bool
  b AT %IX0.1: bool
  c AT %IX0.2: bool
  y AT %QX0.1: bool
END_VAR
LD a
OR b
AND c
ST y
END_PROGRAM

```

Übung 5.11 (POWER52)

Die Lösung entspricht genau „Power51b“!

```

Program POWER52
(*Processes: *)
(* Standard-I/O byte 0 *)
var
  a AT %IX0.0: bool
  b AT %IX0.1: bool
  c AT %IX0.2: bool
  y AT %QX0.0: bool
end_var
LD a
OR b
AND c
ST y
end_program

```

Übung 5.12 (MEMO51)

```

Program Memo51
(*Processes: *)
(* Standard-I/O byte 0 *)
var
  a AT %IX0.0: bool
  b AT %IX0.1: bool
  c AT %IX0.2: bool
  mem : bool
  x AT %QX0.0: bool
  y AT %QX0.1: bool

```

```

    z AT %QX0.2: bool
end_var
(* Term 1 *)
  ld a
  or b
  st mem
  ld c
  and mem
  st x
(* Term 2 *)
  ld a
  or b
  and c
  st y
(* Term 3 *)
  ld c
  and( a
  or b
  )
  st z
end_program

```

Übung 5.13 (EXOR51)

```

PROGRAM EXOR51
(*Processes: *)
(* Standard-I/O byte 0 *)
VAR
  A AT %IX0.6: BOOL
  B AT %IX0.7: BOOL
  X AT %QX0.6: BOOL
END_VAR
LD A
XOR B
ST X
END_PROGRAM

```

Kapitel 6

Schaltungen mit Signalspeichern

Übung 6.1 (POWER61)

```
Program POWER61
var
  a AT %IX0.0: bool
  b AT %IX0.1: bool
  x AT %QX0.0: bool
  y AT %QX0.1: bool
end_var
LD   b
OR   x
ANDN a
ST   x

LD   y
ANDN a
OR   b
ST   y
end_program
```

Übung 6.2 (RS61)

```
Program RS61
(*Processes: *)
(* Standard-I/O byte 0 *)
(* Boiler *)
var
  a AT %IX0.7: bool
  b AT %IX0.6: bool
  x AT %QX0.0: bool
end_var
```

```

ld a
s x
ld b
r x
end_program

```

Übung 6.3 Keine Musterlösung.

Übung 6.4 Keine Musterlösung.

Übung 6.5 (RS62)

```

Program RS62
(*Processes: *)
(* Standard-I/O byte 0 *)
var
  a AT %IX0.7: bool
  b AT %IX0.6: bool
  x AT %QX0.0: bool
  y AT %QX0.2: bool
  Memo1 : bool
  Memo2 : bool
end_var
ld a
s Memo1
ld b
r Memo1
ld Memo1
st x

ld b
r Memo2
ld a
s Memo2
ld Memo2
st y
end_program

```

Übung 6.6 (zu Power61)

Stromlaufplan A: vorrangig rücksetzend

Stromlaufplan B: vorrangig setzend

Übung 6.7 (TANK61)

```

Program Tank61
(*Processes:                               *)
(* Levelling                               *)
VAR
  LIS1 AT %ix0.1: BOOL
  LIS2 AT %ix0.2: BOOL
  V1   AT %qx0.1: BOOL
END_VAR
  LDN  LIS1
  S    V1
  LD   LIS2
  R    V1
END_PROGRAM

```

Übung 6.8 (ALARM61)

```

Program Alarm61
(*Processes:                               *)
(* Boiler - press Heating to cause Fault *)
(*OR                                         *)
(* Standard I/O byte1                      *)
(* Panel                                    *)
VAR
  Quit AT %ix0.6: BOOL
  Fault AT %ix1.0: BOOL
  Horn AT %qx0.7: BOOL
END_VAR
  LD  Fault
  S   Horn
  LD  Quit
  R   Horn
END_PROGRAM

```

Übung 6.9 (ALARM62)

```

Program Alarm62
(*Processes:                               *)
(* Standard-I/O byte 0                    *)
(* Standard-I/O byte 1                    *)
(* Panel                                   *)
VAR
  Tast0 AT %ix0.0: BOOL
  Tast1 AT %ix0.1: BOOL
  Tast2 AT %ix0.2: BOOL
  Quitt0 AT %ix1.0: BOOL

```

```

    Quitt1 AT %ix1.1: BOOL
    Quitt2 AT %ix1.2: BOOL
    Horn   AT %qx0.7: BOOL
    Alarm: BOOL
END_VAR
    LD     Tast0
    OR     Tast1
    OR     Tast2
    S      Alarm

    LD     Quitt0
    OR     Quitt1
    OR     Quitt2
    R      Alarm

    LD     Alarm
    ST     Horn
END_PROGRAM

```

Übung 6.10 (ALARM63)

```

Program Alarm63
(*Processes:                               *)
(* Standard-I/O byte 0                     *)
(* Standard-I/O byte 1                     *)
(* Panel                                    *)
VAR
    Tast0 AT %ix0.0: BOOL
    Tast1 AT %ix0.1: BOOL
    Tast2 AT %ix0.2: BOOL
    Quitt0 AT %ix1.0: BOOL
    Quitt1 AT %ix1.1: BOOL
    Quitt2 AT %ix1.2: BOOL
    Lamp0 AT %qx1.0: BOOL
    Lamp1 AT %qx1.1: BOOL
    Lamp2 AT %qx1.2: BOOL
    Horn AT %qx0.7: BOOL
    Alarm: BOOL
END_VAR
    LD     Tast0
    OR     Tast1
    OR     Tast2
    S      Alarm

    LD     Quitt0
    OR     Quitt1

```

```

OR   Quitt2
R    Alarm
R    Lamp0
R    Lamp1
R    Lamp2

LD   Tast0
S    Lamp0
LD   Tast1
S    Lamp1
LD   Tast2
S    Lamp2

LD   Alarm
ST   Horn
END_PROGRAM

```

Übung 6.11 (ALARM64)

```

program ALARM64
(*Processes: *)
(* Boiler - press Heating to cause Fault *)
(*OR *)
(* Standard I/O byte1 *)
(* Panel *)
var
  y1: rs
  y2: rs
  Quitt AT %ix0.6: bool
  Fault AT %ix1.0: bool
  Lamp AT %qx1.0: bool
  Horn AT %qx0.7: bool
end_var

ld Quitt
and Fault
st y1.s
ldn Fault
st y1.r1

ldn y1.q1
and Fault
st y2.s
ld Quitt
st y2.r1

```

```

cal y1
cal y2

ld y1.q1
or y2.q1
st Lamp
ld y2.q1
st Horn

end_program

```

Übung 6.12 (TANK62)

```

Program Tank62
(*Processes: *)
(* Tanks (small) *)
VAR
  V1FF : RS
  Fill AT %ix0.7: BOOL
  LIS1 AT %ix0.1: BOOL
  LIS2 AT %ix0.2: BOOL
  V1 AT %qx0.1: BOOL
END_VAR
ld Fill
st V1FF.S
ld LIS2
st V1FF.R1

cal V1FF

ld V1FF.Q1
st V1
END_PROGRAM

```

Übung 6.13 (TANK63)

```

Program Tank63
(*Processes: *)
(* Tanks (small) *)
VAR
  V1FF : RS
  V3FF : RS
  Fill AT %ix0.7: BOOL
  Empty AT %ix0.6: BOOL

```



```

    LIS1 AT %ix0.1: BOOL
    LIS2 AT %ix0.2: BOOL
    V1    AT %qx0.1: BOOL
    V3    AT %qx0.3: BOOL
END_VAR
    ld    Fill
    st    V1FF.S
    ld    LIS2
    st    V1FF.R1

    ld    Empty
    st    V3FF.S
    ldn   LIS1
    st    V3FF.R1

    cal   V1FF
    cal   V3FF

    ld    V1FF.Q1
    st    V1

    ld    V3FF.Q1
    st    V3
END_PROGRAM

```

Übung 6.14 (TANK64)

```

Program Tank64
(*Processes:                *)
(* Tanks (small)           *)
VAR
    V1FF : RS
    V3FF : RS
    Fill AT %ix0.7: BOOL
    Empty AT %ix0.6: BOOL
    LIS1 AT %ix0.1: BOOL
    LIS2 AT %ix0.2: BOOL
    V1    AT %qx0.1: BOOL
    V3    AT %qx0.3: BOOL
END_VAR
    ld    Fill
    andn  V3FF.Q1
    st    V1FF.S
    ld    LIS2
    st    V1FF.R1

```

```

ld    Empty
andn  V1FF.Q1
st    V3FF.S
ldn   LIS1
st    V3FF.R1

cal   V1FF
cal   V3FF

ld    V1FF.Q1
st    V1

ld    V3FF.Q1
st    V3
END_PROGRAM

```

Übung 6.15 (TANK65)

```

Program Tank65
(*Processes:                *)
(* Tanks (small)           *)
VAR
  V1FF : RS
  V3FF : RS
  Fill  AT %ix0.7: BOOL
  LIS1  AT %ix0.1: BOOL
  LIS2  AT %ix0.2: BOOL
  V1     AT %qx0.1: BOOL
  V3     AT %qx0.3: BOOL
END_VAR
ld    Fill
andn  V3FF.Q1
st    V1FF.S
ld    LIS2
st    V1FF.R1

ld    LIS2
andn  V1FF.Q1
st    V3FF.S
ldn   LIS1
st    V3FF.R1

cal   V1FF
cal   V3FF

ld    V1FF.Q1

```

```
st    V1

ld    V3FF.Q1
st    V3
END_PROGRAM
```

Übung 6.16 (SWITCH61) Keine Musterlösung.

Kapitel 7

Zeitfunktionen mit SPS

Übung 7.1 (MIXER71)

```
Program Mixer71
(*Processes:                               *)
(* Boiler                                  *)
var
  Start AT %ix0.7: BOOL
  Mixer AT %qx0.6: BOOL
  Impuls: TP
end_var
  ld Start
  st Impuls.IN
  ld t#3000ms
  st Impuls.PT

  cal Impuls

  ld Impuls.Q
  st Mixer
end_program
```

Übung 7.2 (MIXER72)

```
Program Mixer72
(*Processes:                               *)
(* Boiler                                  *)
var
  Start AT %ix0.7: BOOL
  Mixer AT %qx0.6: BOOL
  Impuls: TP
  Lamp AT %q0.0: BOOL
end_var
```

```

ld Start
st Impuls.IN
ld t#3000ms
st Impuls.PT

cal Impuls

ld Impuls.Q
st Mixer
st Lamp
end_program

```

Übung 7.3 (MIXER73)

```

Program Mixer73
(*Processes: *)
(* Boiler *)
var
  Start AT %ix0.7: BOOL
  Stop AT %ix0.6: BOOL
  Mixer AT %qx0.6: BOOL
  Lamp AT %qx0.0: BOOL
  Impuls: TP
  Run: BOOL
end_var
ld Start
s Run
ld Stop
r Run

ld Start
st Impuls.IN
ld t#3000ms
st Impuls.PT

cal Impuls

ld Impuls.Q
or Start
and Run
st Mixer

ld Run
st Lamp
end_program

```

Übung 7.4 (TANK71)

```

Program Tank71
(*Processes: *)
(* Tanks (small) *)
VAR
  V1FF : RS
  V3FF : RS
  Fill AT %ix0.7: BOOL
  Empty AT %ix0.6: BOOL
  LIS1 AT %ix0.1: BOOL
  LIS2 AT %ix0.2: BOOL
  V1 AT %qx0.1: BOOL
  V3 AT %qx0.3: BOOL
  Horn AT %qx0.7: BOOL
  Pause : TP
END_VAR
  ld Fill
  andn V3FF.Q1
  st V1FF.S
  ld LIS2
  st V1FF.R1
  st Pause.IN

  ld t#5000ms
  st Pause.PT
  cal Pause

  ld Pause.Q
  st Horn

  ld Empty
  andn Pause.Q
  andn V1FF.Q1
  st V3FF.S

  ldn LIS1
  st V3FF.R1

  cal V1FF
  cal V3FF

  ld V1FF.Q1
  st V1
  ld V3FF.Q1
  st V3

```

END_PROGRAM

Übung 7.5 (TANK72)

```

Program Tank72
(*Processes: *)
(* Tanks (small) *)
VAR
  V1FF : RS
  V3FF : RS
  Fill AT %ix0.7: BOOL
  Empty AT %ix0.6: BOOL
  LIS1 AT %ix0.1: BOOL
  LIS2 AT %ix0.2: BOOL
  V1 AT %qx0.1: BOOL
  V3 AT %qx0.3: BOOL
  Horn AT %qx0.7: BOOL
  Pause : TP
  TimeAfter: TP
  isEmpty: BOOL
  isFull: BOOL
END_VAR
  ldn LIS1
  st isEmpty

  ld LIS2
  st isFull

  ld Fill
  andn V3FF.Q1
  st V1FF.S
  ld isFull
  st V1FF.R1
  st Pause.IN

  ld t#3s
  st Pause.PT
  cal Pause

  ld Pause.Q
  st Horn

  ld Empty
  andn Pause.Q
  andn V1FF.Q1
  st V3FF.S

```



```

ld   isEmpty
st   TimeAfter.IN

ld   t#3s
st   TimeAfter.PT
cal  TimeAfter

ld   isEmpty
andn TimeAfter.Q
st   V3FF.R1

cal  V1FF
cal  V3FF

ld   V1FF.Q1
st   V1
ld   V3FF.Q1
st   V3
END_PROGRAM

```

Übung 7.6 (FLASH71)

```

program GeneratorERROR_Flash71
(*Processes:                *)
(* Standard-I/O byte 0     *)
var
  Impuls1:      TP
  Impuls2:      TP
  Lamp AT %QX0.0: bool
end_var
ld   t#1000ms    (* Zeiten einstellen      *)
st   Impuls1.pt
st   Impuls2.pt
ldn  Impuls2.q   (* läuft Timer2?      *)
st   Impuls1.in (* wenn nein Timer1 starten *)
ldn  Impuls1.q   (* läuft Timer1?      *)
st   Impuls2.in (* wenn nein Timer2 starten *)
cal  Impuls1     (* Timer aufrufen     *)
cal  Impuls2
ld   Impuls1.q
st   Lamp
end_program

```

Übung 7.7 (FLASH72)

```

program Flash72
(*Processes: *)
(* Standard-I/O byte 0 *)
var
  Impuls1: TP
  Impuls2: TP
  Lamp AT %QX0.0: bool
end_var
  ld t#1000ms (* Zeiten einstellen *)
  st Impuls1.pt
  st Impuls2.pt
  ldn Impuls2.q (* läuft Timer2? *)
  st Impuls1.in (* wenn nein Timer1 starten *)
  cal Impuls1 (* Timer1 aufrufen *)

  ldn Impuls1.q (* läuft Timer1? *)
  st Impuls2.in (* wenn nein Timer2 starten *)
  cal Impuls2 (* Timer2 aufrufen *)

  ld Impuls1.q
  st Lamp
end_program

```

Übung 7.8 (ALARM71)

```

program ALARM71
(*Processes: *)
(* Boiler - press Heating to cause Fault *)
(*OR *)
(* Standard I/O byte1 *)
(* Panel *)
var
  y1: rs
  y2: rs
  Quitt AT %ix0.6: bool
  Fault AT %ix1.0: bool
  Lamp AT %qx1.0: bool
  Horn AT %qx0.7: bool
  Impuls1: TP
  Impuls2: TP
  y3: bool
end_var

  ld Quitt
  and Fault

```

```

st y1.s
ldn Fault
st y1.r1

ldn y1.q1
and Fault
st y2.s
ld Quitt
st y2.r1

cal y1
cal y2

ld t#1250ms
st Impuls1.pt
st Impuls2.pt

ldn Impuls2.q
st Impuls1.in
cal Impuls1
ldn Impuls1.q
st Impuls2.in
cal Impuls2

ld y1.q1
or y3
st Lamp

ld y2.q1
and Impuls1.Q
st y3

ld y3
st Horn

end_program

```

Übung 7.9 (ALARM72)

```

program ALARM72
(*Processes: *)
(* Boiler - press Heating to cause Fault *)
(*OR *)
(* Standard I/O byte1 *)
(* Panel *)
var

```

```
y1: rs
y2: rs
Quitt AT %ix0.6: bool
Fault AT %ix1.0: bool
Lamp AT %qx1.0: bool
Horn AT %qx0.7: bool
Impuls1: TP
Impuls2: TP
Impuls3: TP
end_var

ld Quitt
and Fault
st y1.s
ldn Fault
st y1.r1

ldn y1.q1
and Fault
st y2.s
ld Quitt
st y2.r1

cal y1
cal y2

ld t#1250ms
st Impuls1.pt
st Impuls2.pt
ld t#5s
st Impuls3.pt

ldn Impuls2.q
st Impuls1.in
cal Impuls1
ldn Impuls1.q
st Impuls2.in
cal Impuls2

ld Quitt
st Impuls3.IN
cal Impuls3

ld y2.q1
andn Impuls1.Q
```

```

    or  Impuls3.Q
    st  Lamp

    ld  y2.q1
    and Impuls1.Q
    st  Horn

end_program

```

Übung 7.10 (FLASH73)

```

program Flash73
(*Processes: *)
(* Standard-I/O byte 0 *)
var
  Impuls1:      TP
  Impuls2:      TP
  Impuls3:      TP
  Lamp1  AT %QX0.0: BOOL
  Lamp2  AT %QX0.1: BOOL
  Lamp3  AT %QX0.2: BOOL
end_var
  ld t#1s
  st Impuls1.pt
  st Impuls2.pt
  st Impuls3.pt

  ldn Impuls3.q
  andn Impuls2.q
  st  Impuls1.in
  cal Impuls1

  ldn Impuls1.q
  andn Impuls3.q
  st  Impuls2.in
  cal Impuls2

  ldn Impuls2.q
  andn Impuls1.q
  st  Impuls3.in
  cal Impuls3

  ld  Impuls1.q
  st  Lamp1
  ld  Impuls2.q

```

```

st Lamp2
ld Impuls3.q
st Lamp3
end_program

```

Übung 7.11 (FLASH75)

```

Program Einschaltverz
(*Processes: *)
(* Boiler *)
var
Pulse: TON
Start AT %IX0.0: bool
Lamp AT %QX0.0: bool
end_var
ld Start
st Pulse.IN
ld t#1000ms
st Pulse.PT
cal Pulse
ld Pulse.Q
st Lamp
end_program

```

Übung 7.12 (FLASH76)

```

PROGRAM IMPULSE
(*Processes: *)
(* Standard-I/O byte 0 *)
VAR
PULSE: TON
LAMP AT %QX0.0: BOOL
END_VAR
LDN PULSE.Q
ST PULSE.IN
LD T#500MS
ST PULSE.PT
CAL PULSE
LD PULSE.Q
ST LAMP
END_PROGRAM

```

Übung 7.12 (FLASH76long)

```
Program ImpulseLang
(*Processes: *)
(* Standard-I/O byte 0 *)
var
  LED: TP (* Impulsverlängerer *)
  Pulse: TON
  Lamp AT %QX0.0: bool
end_var
  ldn Pulse.Q (* Ausgang negiert laden und *)
  st Pulse.IN (* auf den Eingang rückkoppeln *)
  ld t#500ms
  st Pulse.PT
  cal Pulse (* Timer starten *)
  ld t#150ms (* Pulsdauer verlängern *)
  st LED.PT
  ld Pulse.Q
  st LED.IN
  cal LED
  ld LED.Q (* Ausgang des LED-Timers *)
  st Lamp
end_program
```


Kapitel 8

Zähler mit SPS

Übung 8.1 (INOUT81)

```
PROGRAM INTEGER
(*Processes: *)
(* Standard-I/O byte 0 *)
(* Hex-Output byte 0 *)
VAR
  VALUE AT %IB0: sint
  OUT AT %QB0: sint
END_VAR
LD VALUE
ST OUT
END_PROGRAM
```

Übung 8.2 (INOUT82)

```
PROGRAM INTEGER
(*Processes: *)
(* Standard-I/O byte 0 *)
(* Standard-I/O byte 1 *)
(* Hex-Input byte 0 *)
(* Hex-Input byte 1 *)
(* Hex-Output byte 0 *)
(* Hex-Output byte 1 *)
(* dword: also bytes 2 & 3 *)
VAR
  VALUE AT %IB0: sint
  OUT AT %QB0: sint
END_VAR
LD VALUE
ST OUT
END_PROGRAM
```

Übung 8.3 (INOUT83)

```

PROGRAM INTEGER
(*Processes:                               *)
(* Standard-I/O byte 0                      *)
(* Standard-I/O byte 1                      *)
(* Hex-Input byte 0                         *)
(* Hex-Input byte 1                         *)
(* Hex-Output byte 0                        *)
(* Hex-Output byte 1                        *)
(* dword: also bytes 2 & 3 *)
VAR
  VALUE AT %IB0: usint
  OUT AT %QB0: sint
END_VAR
LD VALUE
usint_to_sint
ST OUT
END_PROGRAM

```

Übung 8.4 (COUNT81)

```

PROGRAM CountUP
(*Processes:                               *)
(* Counter CTU                             *)
(* Hex-Input byte 1                         *)
(* Hex-Output byte 1                        *)
VAR
  Counter : CTU
  Clock AT %IX0.3: Bool
  Reset AT %IX0.0: Bool
  ComparePV AT %QX0.3: Bool
  PresetValue AT %IB1: SINT
  CountValue AT %QB1: SINT
END_VAR
LD Clock
ST Counter.CU
LD PresetValue
SINT_TO_INT (* Typumwandlung! *)
ST Counter.PV
LD Reset
ST Counter.R
CAL Counter (* Zähler aufrufen *)
LD Counter.Q
ST ComparePV

```

```

LD Counter.CV
INT_TO_SINT (* Typumwandlung! *)
ST CountValue
END_PROGRAM

```

Übung 8.5 (COUNT82)

```

PROGRAM Countdown
(*Processes: *)
(* Counter CTD *)
(* Hex-Input byte 1 *)
(* Hex-Output byte 1 *)
VAR
Counter : CTD
Clock AT %IX0.2: Bool
Load AT %IX0.1: Bool
ComparePV AT %QX0.2: Bool
PresetValue AT %IB1: SINT
CountValue AT %QB1: SINT
END_VAR
LD Clock
ST Counter.CD
LD PresetValue
sint_to_int
ST Counter.PV
LD Load
ST Counter.LD

CAL Counter

LD Counter.Q
ST ComparePV
LD Counter.CV
int_to_sint
ST CountValue
END_PROGRAM

```

Übung 8.6 (COUNT83)

```

PROGRAM CountUPDN
(*Processes: *)
(* Counter CTUD *)
(* Hex-Input byte 1 *)

```

```

(* Hex-Output   byte 1   *)
VAR
  Counter : CTUD
  ClockDN  AT %IX0.2: Bool
  ClockUP  AT %IX0.3: Bool
  Reset    AT %IX0.0: Bool
  SetLoad  AT %IX0.1: Bool
  CompareZero AT %QX0.2: Bool
  ComparePV AT %QX0.3: Bool
  PresetValue AT %IB1: SINT
  CountValue AT %QB1: SINT
END_VAR

LD PresetValue
SINT_TO_INT (* Typumwandlung! *)
ST Counter.PV
LD ClockDN
ST Counter.CD
LD ClockUP
ST Counter.CU
LD Reset
ST Counter.R
LD SetLoad
ST Counter.LD

CAL Counter

LD Counter.QU
ST ComparePV
LD Counter.QD
ST CompareZero
LD Counter.CV
INT_TO_SINT (* Typumwandlung! *)
ST CountValue
END_PROGRAM

```

Übung 8.7 (COUNT84)

```

PROGRAM Count84
(*Processes: *)
(* Standard-I/O byte 0 *)
(* Hex-Output   byte 1   *)
VAR
  Counter : CTUD
  ClientOUT AT %IX0.0: Bool

```

```

ClientIN  AT %IX0.1: Bool
NoClient  AT %QX0.0: Bool
Client1to5 AT %QX0.1: Bool
MoreThanFive AT %QX0.2: Bool
CountValue AT %QB1: SINT
END_VAR
LD 5
ST Counter.PV
LD ClientOUT
ST Counter.CD
LD ClientIN
ST Counter.CU

CAL Counter

LD Counter.QU
ST MoreThanFive
LD Counter.QD
ST NoClient

LD MoreThanFive
XOR NoClient
STN Client1to5
LD Counter.CV
INT_TO_SINT (* Typumwandlung! *)
ST CountValue
END_PROGRAM

```

Übung 8.8 (DEKADE81)

```

PROGRAM Dekade81
(*Processes: *)
(* Standard-I/O byte 0 *)
(* Standard-I/O byte 1 *)
(* Standard-I/O byte 2 *)
(* Standard-I/O byte 3 *)
(* Hex-Output byte 1 *)
(* Hex-Output byte 2 *)
(* Hex-Output byte 3 *)
VAR
One : CTU
Ten : CTU
Hun : CTU
Clock AT %IX0.3: Bool
Reset AT %IX0.0: Bool

```

```

ByteOne AT %QB1: SINT
ByteTen AT %QB2: SINT
ByteHun AT %QB3: SINT

END_VAR
LD 10
ST One.PV
ST Ten.PV
ST Hun.PV
LD Clock
ST One.CU

CAL One
LD One.CV
int_to_sint
ST ByteOne
LD One.Q
ST Ten.CU
OR Reset
ST One.R

CAL Ten
LD Ten.CV
int_to_sint
ST ByteTen
LD Ten.Q
ST Hun.CU
OR Reset
ST Ten.R

CAL Hun
LD Hun.CV
int_to_sint
ST ByteHun
LD Hun.Q
OR Reset
ST Hun.R

END_PROGRAM

```

Übung 8.9 (MIXER81)

```

Program Mixer81
(*Processes: *)
(* Chemical Process(small) *)

```

```

(* - OR - Tanks (small) *)
VAR
  V1FF : RS
  V3FF : RS
  Start AT %ix0.7: BOOL
  Stop  AT %ix0.6: BOOL
  LIS1  AT %ix0.1: BOOL
  LIS2  AT %ix0.2: BOOL
  V1     AT %qx0.1: BOOL
  V3     AT %qx0.3: BOOL
  Lamp  AT %qx0.0: BOOL
  Value AT %qb3: SINT
  Run   : BOOL
  Fill  : BOOL
  Counter: CTD
END_VAR
  ld  3
  st  Counter.PV

  ld  Start
  and Counter.Q
  S   Run
  S   Fill
  st  Counter.LD

  cal Counter

  ld  Counter.Q
  R   Fill
  ld  Counter.CV
  int_to_sint
  st  Value

  ld  Fill
  andn V3FF.Q1
  st  V1FF.S
  ld  LIS2
  st  V1FF.R1

  ld  LIS2
  andn V1FF.Q1
  st  V3FF.S
  ldn LIS1
  st  V3FF.R1
  st  Counter.CD

```

```

cal V1FF
cal V3FF

ld V1FF.Q1
st V1

ld V3FF.Q1
st V3

ld Run
st Lamp
END_PROGRAM

```

Übung 8.10 (GEN81)

```

Program ImpulseGEN81
(*Processes: *)
(* Hex-Output byte 3 *)
var
  Display AT %qb3: SINT
  Zaehler: CTU
  Pulse: TON
end_var
(* Zaehler *)
ld Pulse.Q
st Zaehler.CU

(* Impulsgenerator *)
ldn Pulse.Q
st Pulse.IN
ld t#500ms
st Pulse.PT

cal Zaehler
cal Pulse

ld Zaehler.CV
int_to_sint
st Display
end_program

```

Übung 8.11 (GEN82)

```

Program ImpulseGEN82

```



```

(*Processes: *)
(* Standard-I/O byte 0 *)
(* Hex-Output byte 3 *)
var
  Display AT %qb3: SINT
  Counter: CTU
  Pulse: TON
  Stopp AT %i0.7: BOOL
end_var
(* Zaehler *)
  ld Pulse.Q
  st Counter.CU

(* Impulsgenerator *)
  ldn Pulse.Q
  andn Stopp
  st Pulse.IN
  ld t#100ms
  st Pulse.PT

  cal Counter
  cal Pulse

  ld Counter.CV
  int_to_sint
  st Display
end_program

```

Übung 8.12 (GEN83)

```

Program ImpulseGEN83
(*Processes: *)
(* Standard-I/O byte 0 *)
(* Hex-Output byte 3 *)
(* - OR - *)
(* Chemical Process (small)*)
var
  Display AT %qb3: SINT
  Counter: CTUD
  Pulse: TON
  Pulse2:TON
  runUP AT %i0.7: BOOL
  runDN AT %i0.6: BOOL
end_var
(* Zaehler *)
  ld Pulse.Q

```

```

    st Counter.CU
    ld Pulse2.Q
    st Counter.CD

(* Impulsgenerator *)
    ldn Pulse.Q
    and runUP
    st Pulse.IN
    ld t#100ms
    st Pulse.PT

(* Impulsgenerator2 *)
    ldn Pulse2.Q
    and runDN
    st Pulse2.IN
    ld t#100ms
    st Pulse2.PT

    cal Counter
    cal Pulse
    cal Pulse2

    ld Counter.CV
    int_to_sint
    st Display
end_program

Program ImpulseGEN83b
(*Processes: *)
(* Standard-I/O byte 0 *)
(* Hex-Input byte 3 *)
(* Hex-Output byte 3 *)
var
    Display AT %qb3: SINT
    MaxVal AT %ib3: SINT
    Counter: CTUD
    Pulse: TON
    Pulse2:TON
    runUP AT %i0.7: BOOL
    runDN AT %i0.6: BOOL
end_var
(* Zaehler *)
    ld Pulse.Q
    st Counter.CU
    ld Pulse2.Q

```

```

    st Counter.CD
    ld MaxVal
    sint_to_int
    st Counter.PV

(* Impulsgenerator *)
    ldn Pulse.Q
    and runUP
    andn Counter.QU
    st Pulse.IN
    ld t#100ms
    st Pulse.PT

(* Impulsgenerator2 *)
    ldn Pulse2.Q
    and runDN
    andn Counter.QD
    st Pulse2.IN
    ld t#100ms
    st Pulse2.PT

    cal Counter
    cal Pulse
    cal Pulse2

    ld Counter.CV
    int_to_sint
    st Display
end_program

```

Übung 8.13 (TIME81)

```

Program Time81
(*Processes: *)
(* Standard-I/O byte 0 *)
(* Hex-Output byte 3 *)
var
    L1 AT %ix0.1: BOOL
    L2 AT %ix0.2: BOOL
    Stop AT %ix0.6: BOOL
    SW1 AT %ix0.0: BOOL
    Display AT %qb3: SINT
    Counter: CTU
    Pulse: TON
    count: bool

```

```

end_var
(* Zaehler *)
  ld Pulse.Q
  st Counter.CU

(* Starten *)
  ld L1
  s count
(* Stoppen *)
  ld L2
  r count
(* Zaehler Reset *)
  ld Stop
  or SW1
  st Counter.R

(* Impulsgenerator *)
  ldn Pulse.Q
  and count (* Lauf *)
  st Pulse.IN
  ld t#200ms
  st Pulse.PT

cal Counter
cal Pulse

ld Counter.CV
int_to_sint
st Display
end_program

```

Übung 8.14 (TIME82)

```

Program FillTimeCountTime82
(*Processes: *)
(* Chemical Process (small)*)
var
  LIS1 AT %ix0.1: BOOL
  LIS2 AT %ix0.2: BOOL
  Start AT %ix0.7: BOOL
  Stop AT %ix0.6: BOOL
  SW1 AT %ix0.0: BOOL
  Display AT %qb3: SINT
  V1 AT %qx0.1: BOOL
  V3 AT %qx0.3: BOOL
  Counter: CTU

```

```
Pulse: TON
count: bool
run: bool
end_var
(* Starten *)
  ld Start
  s run
  r count
(* Stoppen *)
  ld Stop
  r run
(* Fuellen *)
  ld run
  st V1
(* Leeren *)
  ldn run
  st V3

(* Zaehler *)
  ld Pulse.Q
  st Counter.CU

(* Starten *)
  ld LIS1
  s count
(* Stoppen *)
  ld LIS2
  r count
(* Zaehler Reset *)
  ld Stop
  or SW1
  st Counter.R

(* Impulsgenerator *)
  ldn Pulse.Q
  and run
  and count (* Lauf *)
  st Pulse.IN
  ld t#10ms
  st Pulse.PT

cal Counter
cal Pulse

ld Counter.CV
```

```

    int_to_sint
    st Display
end_program

```

Übung 8.15 (TANK81)

```

Program Tank81
(*Processes: *)
(* Tanks (small) *)
var
    SW1    AT %ix0.0: BOOL
    Start AT %ix0.7: BOOL
    Stop   AT %ix0.6: BOOL
    LIS1   AT %ix0.1: BOOL
    LIS2   AT %ix0.2: BOOL
    V1     AT %qx0.1: BOOL
    V3     AT %qx0.3: BOOL
    Display AT %qb3: SINT

    Zaehler: CTU
    Pulse: TON
    count: bool
    run: bool
end_var
(* Zaehler *)
    ld Pulse.Q
    st Zaehler.CU

(* Starten *)
    ld LIS1
    and run
    s count
    ld Start
    s run
(* Stoppen *)
    ld LIS2
    r count
    ld Stop
    r run
(* Zaehler Reset *)
    ld SW1
    st Zaehler.R
    r count

(* Fuellen *)

```

```

    ld run
    st V1
(* Leeren *)
    ldn run
    st V3

(* Impulsgenerator *)
    ldn Pulse.Q
    and count (* Lauf *)
    st Pulse.IN
    ld 30
    st Pulse.PT

    cal Zaehler
    cal Pulse

    ld Zaehler.CV
    int_to_sint
    st Display
end_program

```

Übung 8.16 (REAKT81)

```

Program Reaktion
(* Nach Druck auf Starttaster *)
(* leuchtet nach Vorlaufzeit *)
(* Led2 an qx0.6 auf. *)
(* Gleichzeitig startet die Zeit*)
(* Druck auf Stoptaster stoppt*)
(* die Reaktionszeit *)
(*Processes: *)
(* Standard-I/O byte 0 *)
(* Hex-Output byte 3 *)
var
    Start AT %ix0.7: BOOL
    Stop AT %ix0.6: BOOL
    SW1 AT %ix0.0: BOOL
    Display AT %qb3: SINT
    Led1 AT %qx0.7: BOOL
    Led2 AT %qx0.6: BOOL
    Counter: CTU
    Pulse: TON
    count: bool
    run: bool

```

```
Vorlauf: TP
end_var
(* Zaehler *)
  ld Pulse.Q
  st Counter.CU
(* Starten *)
  ldn Vorlauf.Q
  and run
  s count
  ld Start
  s run
(* Stoppen *)
  ld Stop
  r count
  r run
(* Zähler Reset *)
  ld Start
  st Counter.R
(* Vorlaufzeit *)
  ld run
  st Vorlauf.IN
  ldn Vorlauf.Q
  stn Led1
  and run
  st Led2
  ld 3000
  st Vorlauf.pt
(* Impulsgenerator *)
  ldn Pulse.Q
  and count (* Lauf *)
  st Pulse.IN
  ld t#1ms
  st Pulse.PT

cal Counter
cal Pulse
cal Vorlauf

ld Counter.CV
int_to_sint
st Display

end_program
```


Kapitel 9

Funktionsbausteine

Übung 9.1

```
program Flash72
var
  Impuls1:          TP
  Impuls2:          TP
  Lamp AT %QX0.0: bool
end_var
  ld  t#1000ms      (* Zeiten einstellen          *)
  st  Impuls1.pt
  st  Impuls2.pt

  ldn Impuls2.q     (* läuft Timer2?              *)
  st  Impuls1.in   (* wenn nein Timer1 starten *)
  cal Impuls1      (* Timer1 aufrufen          *)

  ldn Impuls1.q     (* läuft Timer1?              *)
  st  Impuls2.in   (* wenn nein Timer2 starten *)
  cal Impuls2      (* Timer2 aufrufen          *)

  ld  Impuls1.q
  st  Lamp
end_program
```

```
FUNCTION_BLOCK Gen05
```

```
VAR
  Impuls1 : TP
  Impuls2 : TP
END_VAR
VAR_OUTPUT
  Y : BOOL
END_VAR
```

```

LD    t#500ms
ST    Impuls1.PT
ST    Impuls2.PT

LDN   Impuls2.Q
ST    Impuls1.IN
CAL   Impuls1

LDN   Impuls1.Q
ST    Impuls2.IN
CAL   Impuls2

LD    Impuls1.Q
ST    Y
RET
END_FUNCTION_BLOCK

```

Übung 9.2 (FLASH92)

```

program FlashLightFlash92
(*Processes: *)
(* Standard-I/O byte 0 *)
var
  Flash: Gen05
  Lamp AT %qx0.0: Bool
end_var
  CAL Flash
  LD Flash.Y
  ST Lamp
end_program

```

Übung 9.3 (GEN91)

```

Program ImpulseGen91
(*Processes: *)
(* Hex-Output byte 3 *)
var
  Display AT %qb3: SINT
  Counter: CTU
  Pulse: Sec1
end_var
(* Counter *)
  ld Pulse.Y
  st Counter.CU

```

```

(* Impulsgenerator *)
  cal Pulse
  cal Counter

  ld Counter.CV
  int_to_sint
  st Display
end_program

---

Function_Block Sec1
var
  Pulse: TON
end_var
var_output
  Y: Bool
end_var
(* Impulsgenerator *)
  ldn Pulse.Q
  st Pulse.IN
  ld t#1s
  st Pulse.PT
  cal Pulse
  ld Pulse.Q
  st Y
end_function_block

```

Übung 9.4 (ALARM91)

```

Program Alarm91
(*Processes: *)
(* Boiler - press Heating to cause Fault *)
(*OR *)
(* Standard I/O byte1 *)
(* Panel *)
VAR
  Quit AT %ix0.6: BOOL
  Fault AT %ix1.0: BOOL
  Horn AT %qx0.7: BOOL
  Blink: Gen05
  Lamp AT %qx1.0: BOOL
END_VAR
LD Fault
S Horn

```

```

LD    Quit
R     Horn
CAL  Blink
LD    Horn
AND  Blink.Y
ST    Lamp
END_PROGRAM

```

Übung 9.5 Keine Musterlösung.

Übung 9.6 (FFFB92)

```

(* FUNCTION BLOCK *)
FUNCTION_BLOCK FFSR
VAR_INPUT
  Set   : BOOL
  Rset  : BOOL
END_VAR
VAR_OUTPUT
  Y     : BOOL
END_VAR
LD     Set
ORN(   Rset
AND    Y
)
ST     Y
RET
END_FUNCTION_BLOCK

```

```

program FFFB92
(*Processes: *)
(* Standard-I/O byte 0 *)
var
  FF: FFSR
  RSet AT %ix0.0: BOOL
  Set  AT %ix0.1: BOOL
  Out  AT %qx0.0: BOOL
end_var
LD  Set
ST  FF.Set
LD  RSet
ST  FF.RSet

CAL FF

```

```
LD FF.Y
ST Out
end_program
```

Übung 9.7 (FFFB93)

```
(* FUNCTION BLOCK *)
FUNCTION_BLOCK FFRS
VAR_INPUT
  Set   : BOOL
  Rset  : BOOL
END_VAR
VAR_OUTPUT
  Y     : BOOL
END_VAR
LDN RSet
AND( Set
OR   Y
)
ST   Y
RET
END_FUNCTION_BLOCK
```

Übung 9.8 (TANK91)

```
FUNCTION_BLOCK Tank
VAR_INPUT
  LIS1 : BOOL
  LIS2 : BOOL
  Start: BOOL
END_VAR
VAR_OUTPUT
  V1 : BOOL
  V3 : BOOL
END_VAR
VAR
  V1FF : RS
  V3FF : RS
END_VAR
LD   Start
ANDN V3
ANDN LIS2
ST   V1FF.S
LD   LIS2
```

```

    ST    V1FF.R1
    ST    V3FF.S
    LDN   LIS1
    ST    V3FF.R1
    cal   V1FF
    cal   V3FF
    ld    V3FF.Q1
    st    V3
    ld    V1FF.Q1
    st    V1
END_FUNCTION_BLOCK

program OneTank
(*Processes:                *)
(* Tanks (small)           *)
var
(* Instanziierung *)
    Tank0: Tank
    LIS01 AT %IX0.1: bool
    LIS02 AT %IX0.2: bool
    V01   AT %QX0.1: bool
    V03   AT %QX0.3: bool
    Start AT %IX0.7: bool
end_var

(* Verknuepfung der Eingangsklemmen *)
    ld Start
    st Tank0.Start
    ld LIS01
    st Tank0.LIS1
    ld LIS02
    st Tank0.LIS2

(* Funktionsbausteinaufruf *)
    cal Tank0

(* Verknuepfung der Ausgangsklemmen *)
    ld Tank0.V1
    st V01
    ld Tank0.V3
    st V03

end_program

```

Übung 9.9 (TANK92)

```

program ThreeTanks
  (*Processes: *)
  (* Tanks (big) *)
var
  (* Instanziierung *)
  Tank0: Tank
  LIS01 AT %IX0.1: bool
  LIS02 AT %IX0.2: bool
  V01 AT %QX0.1: bool
  V03 AT %QX0.3: bool
  Tank1: Tank
  LIS11 AT %IX1.1: bool
  LIS12 AT %IX1.2: bool
  V11 AT %QX1.1: bool
  V13 AT %QX1.3: bool
  Tank2: Tank
  LIS21 AT %IX2.1: bool
  LIS22 AT %IX2.2: bool
  V21 AT %QX2.1: bool
  V23 AT %QX2.3: bool
  Start AT %IX0.7: bool
end_var

  (* Verknuepfung der Eingangsklemmen *)
  ld Start
  st Tank0.Start
  ld LIS01
  st Tank0.LIS1
  ld LIS02
  st Tank0.LIS2
  (* Funktionsbausteinaufruf *)
  cal Tank0

  ld Start
  st Tank1.Start
  ld LIS11
  st Tank1.LIS1
  ld LIS12
  st Tank1.LIS2
  (* Funktionsbausteinaufruf *)
  cal Tank1

  ld Start

```

```
    st Tank2.Start
    ld LIS21
    st Tank2.LIS1
    ld LIS22
    st Tank2.LIS2
(* Funktionsbausteinaufruf *)
    cal Tank2

(* Verknuepfung der Ausgangsklemmen *)
    ld Tank0.V1
    st V01
    ld Tank0.V3
    st V03
    ld Tank1.V1
    st V11
    ld Tank1.V3
    st V13
    ld Tank2.V1
    st V21
    ld Tank2.V3
    st V23

end_program
```


Kapitel 10

Sprünge, Schleifen und Wiederholungen

Übung 10.1 (FLASH101)

```
Program flash101
(*Processes: *)
(* Standard-I/O byte 1 *)
(* Hex-Output byte 1 *)
var
  Pulse: TON
  Cycle1: bool
  Bit0 AT %QX1.0: bool
  Byte1 AT %QB1: usint
end_var
(* set Bit *)
  ldn Cycle1
  s Cycle1
  s Bit0

(* Pulsgenerator *)
  ldn Pulse.Q
  st Pulse.IN
  ld t#1000ms
  st Pulse.PT
  cal Pulse

(* Go!! *)
  ldn Pulse.Q
  jmpc Pulse.OK
  ld Byte1
  mul 2
  st Byte1
Pulse.OK:
end_program
```

Übung 10.2 (FLASH102)

```

Program FlashLightFlash102
(*Processes:                               *)
(* Standard-I/O   byte 1                   *)
(* Hex-Output     byte 1                   *)
var
  Pulse: TON
  Cycle1: bool
  Bit0 AT %QX1.0: bool
  Bit7 AT %QX1.7: bool
  Byte1 AT %QB1: usint
end_var
(* set Bit *)
  ldn Cycle1
  s Cycle1
  s Bit0

(* Pulsgenerator *)
  ldn Pulse.Q
  st Pulse.IN
  ld t#1000ms
  st Pulse.PT
  cal Pulse

(* Go!! *)
  ldn Pulse.Q
  jmpc PulseOK

  ld Byte1
  eq 128
  r Bit7
  r Cycle1

  ld Byte1
  mul 2
  st Byte1
PulseOK:
end_program

```

Übung 10.3 (FLASH103)

```

Program Flash103
(*Processes:                               *)
(* Standard-I/O   byte 1                   *)

```

```

(* Hex-Output      byte 1      *)
var
  Pulse: TON
  Cycle1: bool
  Bit7 AT %QX1.7: bool
  Byte1 AT %QB1: usint
end_var
(* set Bit *)
  ldn Cycle1
  s Cycle1
  s Bit7

(* Pulsgenerator *)
  ldn Pulse.Q
  st Pulse.IN
  ld t#1000ms
  st Pulse.PT
  cal Pulse

(* Go!! *)
  ldn Pulse.Q
  jmpc PulseOK
  ld Byte1
  div 2
  st Byte1
  eq 0
  s Bit7
PulseOK:
end_program

```

Übung 10.4 (FLASH104)

```

Program Flash104
(*Processes:                                     *)
(* Standard-I/O  byte 1                          *)
(* Hex-Output    byte 1                          *)
var
  Pulse: TON
  Cycle1: bool
  Bit1 AT %QX1.0: bool
  Bit7 AT %QX1.7: bool
  Byte1 AT %QB1: usint
  GoLeft AT %IX1.0: BOOL
end_var
(* set Bit *)

```

```

    ldn Cycle1
    s Cycle1
    s Bit1

(* Pulsgenerator *)
    ldn Pulse.Q
    st Pulse.IN
    ld t#1000ms
    st Pulse.PT
    cal Pulse

(* Go!! *)
    ldn Pulse.Q
    jmpc PulseOK
    ld GoLeft
    jmpcn RunRight
RunLeft:
    ld Byte1
    eq 128
    r Bit7
    r Cycle1

    ld Byte1
    mul 2
    st Byte1
    jmp PulseOK
RunRight:
    ld Byte1
    div 2
    st Byte1
    eq 0
    s Bit7
PulseOK:
end_program

```

Übung 10.5 Keine Musterlösung.

Übung 10.6 (TANK102)

```

program Tank102_ThreeTanks
(*Processes: *)
(* Tanks (big) *)
var
(* Instanziierung *)
    Tank0: Tank

```

```

LIS01 AT %IX0.1: bool
LIS02 AT %IX0.2: bool
V01   AT %QX0.1: bool
V03   AT %QX0.3: bool
Tank1: Tank
LIS11 AT %IX1.1: bool
LIS12 AT %IX1.2: bool
V11   AT %QX1.1: bool
V13   AT %QX1.3: bool
Tank2: Tank
LIS21 AT %IX2.1: bool
LIS22 AT %IX2.2: bool
V21   AT %QX2.1: bool
V23   AT %QX2.3: bool
Start AT %IX0.7: bool
end_var

(* Verknuepfung der Eingangsklemmen *)
ld Start
st Tank0.Start
ld LIS01
st Tank0.LIS1
ld LIS02
st Tank0.LIS2
(* Funktionsbausteinaufruf *)
cal Tank0

ld Tank0.LIS2
st Tank1.Start
ld LIS11
st Tank1.LIS1
ld LIS12
st Tank1.LIS2
(* Funktionsbausteinaufruf *)
cal Tank1

ld Tank1.LIS2
st Tank2.Start
ld LIS21
st Tank2.LIS1
ld LIS22
st Tank2.LIS2
(* Funktionsbausteinaufruf *)
cal Tank2

```

```

(* Verknuepfung der Ausgangsklemmen *)
  ld Tank0.V1
  st V01
  ld Tank0.V3
  st V03
  ld Tank1.V1
  st V11
  ld Tank1.V3
  st V13
  ld Tank2.V1
  st V21
  ld Tank2.V3
  st V23

end_program

```

Übung 10.7 (7SEG101)

```

Program SevenSegment
(*Processes: *)
(* Standard-I/O byte 1 *)
(* 7-Segment *)
var
  InByte AT %IB1: Byte
  OutByte AT %QB0: Byte
end_var
  ld InByte
  st OutByte
end_program

```

Übung 10.8 (7SEG102)

```

Program SevenSegment
(*Processes: *)
(* Standard-I/O byte 1 *)
(* Hex-Input byte 1 *)
(* 7-Segment *)
Var
  InValue AT %IB1: sint
  OutByte AT %QB0: Byte
  Digit: sint
end_var
  ld InValue

```

```
st Digit
eq 0
jmpc Zero
ld Digit
eq 1
jmpc One
ld Digit
eq 2
jmpc Two
ld Digit
eq 3
jmpc Three
ld Digit
eq 4
jmpc Four
ld Digit
eq 5
jmpc Five
ld Digit
eq 6
jmpc Six
ld Digit
eq 7
jmpc Seven
ld Digit
eq 8
jmpc Eight
ld Digit
eq 9
jmpc Nine
ld Digit
eq 16#a
jmpc _A
ld Digit
eq 16#b
jmpc _B
ld Digit
eq 16#c
jmpc _C
ld Digit
eq 16#d
jmpc _D
ld Digit
eq 16#e
jmpc _E
```

```
    ld Digit
    eq 16#f
    jmpc _F

Zero:
    ld 2#00111111
    jmp End
One:
    ld 2#00000110
    jmp End
Two:
    ld 2#01011011
    jmp End
Three:
    ld 2#01001111
    jmp End
Four:
    ld 2#01100110
    jmp End
Five:
    ld 2#01101101
    jmp End
Six:
    ld 2#01111101
    jmp End
Seven:
    ld 2#00000111
    jmp End
Eight:
    ld 2#01111111
    jmp End
Nine:
    ld 2#01101111
    jmp End
_A:
    ld 2#01110111
    jmp End
_B:
    ld 2#01111100
    jmp End
_C:
    ld 2#00111001
    jmp End
_D:
    ld 2#01011110
```



```
    jmp End
_E:
    ld 2#01111001
    jmp End
_F:
    ld 2#01110001
    jmp End

End:
    st OutByte
end_program
```

Übung 10.9 (DICE101)

```
Function_Block Chance16
var_input
    run: bool
end_var
var_output
    Value: sint
end_var
var
    Counter: CTU
    toggle: bool
end_var

    ldn run
    jmpc ausgabe

    ldn toggle
    st toggle
    st Counter.CV
    cal Counter

    ld Counter.cv
    gt 5
    st Counter.r
    cal Counter
ausgabe:
    ld Counter.CV
    int_to_sint
    add 1
    st Value
end_function_block
```

```
Program ProgDice101
(*Processes: *)
(* Standard-I/O byte 0 *)
(* Hex-Output *)
var
  Start AT %ix0.0: BOOL
  OutByte AT %qb0: sint
  Dice: Chance16
end_var
  ld Start
  st Dice.run
  cal Dice
  ld Dice.Value
  st OutByte
end_program
```

Kapitel 11

Funktionen

Übung 11.1 Keine Musterlösung.

Übung 11.2 (7SEG111)

```
Function int_to_7seg : Byte
var_input
  Digit: int
end_var
  ld Digit
  eq 0
  jmpc Zero
  ld Digit
  eq 1
  jmpc One
  ld Digit
  eq 2
  jmpc Two
  ld Digit
  eq 3
  jmpc Three
  ld Digit
  eq 4
  jmpc Four
  ld Digit
  eq 5
  jmpc Five
  ld Digit
  eq 6
  jmpc Six
  ld Digit
  eq 7
  jmpc Seven
```

```
    ld Digit
    eq 8
    jmpc Eight
    ld Digit
    eq 9
    jmpc Nine
    ld Digit
    eq 16#a
    jmpc _A
    ld Digit
    eq 16#b
    jmpc _B
    ld Digit
    eq 16#c
    jmpc _C
    ld Digit
    eq 16#d
    jmpc _D
    ld Digit
    eq 16#e
    jmpc _E
    ld Digit
    eq 16#f
    jmpc _F

Zero:
    ld 2#00111111
    jmp End
One:
    ld 2#00000110
    jmp End
Two:
    ld 2#01011011
    jmp End
Three:
    ld 2#01001111
    jmp End
Four:
    ld 2#01100110
    jmp End
Five:
    ld 2#01101101
    jmp End
Six:
    ld 2#01111101
```

```

        jmp End
Seven:
        ld 2#00000111
        jmp End
Eight:
        ld 2#01111111
        jmp End
Nine:
        ld 2#01101111
        jmp End
_A:
        ld 2#01110111
        jmp End
_B:
        ld 2#01111100
        jmp End
_C:
        ld 2#00111001
        jmp End
_D:
        ld 2#01011110
        jmp End
_E:
        ld 2#01111001
        jmp End
_F:
        ld 2#01110001
        jmp End

End:
        st int_to_7seg
        ret

end_function

```

```

Program SevenSegment111
(*Processes: *)
(* Standard-I/O byte 0 *)
(* Hex-Input byte 0 *)
(* 7-Segment byte 0 *)
var
    InByte0 AT %IB0: byte
    OutByte0 AT %QB0: byte
end_var

```

```

    ld InByte0
    byte_to_int
    int_to_7seg
    st OutByte0
end_program

```

Übung 11.3 (DICE111)

```

Function int_to_dice : Byte
var_input
  Digit: int
end_var
  ld Digit
  eq 1
  jmpc One
  ld Digit
  eq 2
  jmpc Two
  ld Digit
  eq 3
  jmpc Three
  ld Digit
  eq 4
  jmpc Four
  ld Digit
  eq 5
  jmpc Five
  ld Digit
  eq 6
  jmpc Six
  jmp Fault
One:
  ld 2#01000000
  jmp End
Two:
  ld 2#00001001
  jmp End
Three:
  ld 2#01100100
  jmp End
Four:
  ld 2#00101101
  jmp End
Five:
  ld 2#01101101

```

```

    jmp End
Six:
    ld 2#00111111
    jmp End
Fault:
    ld 0
End:
    st int_to_dice
    ret
end_function

```

```

Program DiceProg111
(*Processes:                *)
(* Panel                    *)
(* Dice          byte 1    *)
var
    Start AT %ix0.0: BOOL
    OutValue AT %qb3: sint
    OutDice AT %qb1: BYTE
    Dice: Chance16
end_var
    ld Start
    st Dice.run
    cal Dice
    ld Dice.Value
    st OutValue
    int_to_dice
    st OutDice
end_program

```

Übung 11.4 (BCD111)

```

(* FUNCTION *)
Function hex_to_bcd: Byte
var_input
    Digit: int
end_var
var
    BCDDigitLow: int
    BCDDigitHigh: int
    BCDByteLow: byte
end_var
    ld 0
    st BCDDigitHigh

```

```

    ld    Digit
    st    BCDDigitLow
gt100:
    lt    100
    jmpc  lt100
    ld    BCDDigitLow
    sub   100
    st    BCDDigitLow
    jmp   gt100
lt100:
    ld    BCDDigitLow
    lt    10
    jmpc  lt10
    ld    BCDDigitLow
    sub   10
    st    BCDDigitLow
    ld    BCDDigitHigh
    add   1
    st    BCDDigitHigh
    ld    BCDDigitLow
    jmp   lt100
lt10:
    ld    BCDDigitLow
    int_to_byte
    st    BCDByteLow
    ld    BCDDigitHigh
    mul   16
    int_to_byte
    or    BCDByteLow
    st    hex_to_bcd
    ret
end_function

```

Program Mengennenmessung

```

(*Processes:                *)
(* Tank (small)             *)
(* Hex-Output      byte 2   *)
var
  Switch AT %ix0.0: BOOL
  Start  AT %ix0.7: BOOL
  Stop   AT %ix0.6: BOOL
  LIS1   AT %ix0.1: BOOL
  LIS2   AT %ix0.2: BOOL
  V1     AT %qx0.1: BOOL

```



```
V3      AT %qx0.3: BOOL
Display AT %qb3: BYTE
HexDisplay AT %qb2: BYTE
Zaehler: CTU
Pulse: TON
count: bool
run: bool
end_var
(* Counter *)
  ld Pulse.Q
  st Zaehler.CU

(* Start *)
  ld LIS1
  and run
  s count
  ld Start
  s run
(* Stopp *)
  ld LIS2
  r count
  ld Stop
  r run
(* Counter Reset *)
  ld Stop
  r run
//  st Zaehler.R
  r count
(* Fill *)
  ld run
  st V1
(* Leeren *)
  ld Switch
  st V3
(* Generator *)
  ldn Pulse.Q
  and count (* Lauf *)
  st Pulse.IN
  ld 60
  st Pulse.PT

cal Zaehler
cal Pulse

ld Zaehler.CV
```

```

hex_to_bcd
st Display
ld Zaehler.CV
int_to_byte
st HexDisplay
end_program

```

Übung 11.5 (MAX111)

Beachten Sie bei dieser Aufgabe, dass die Funktion mit INT-Werten arbeitet. Diese sind 2 Bytes groß; daher werden für die Eingaben zwei Elemente benötigt, nämlich z.B. %ib0 und %ib1 für das „Digit1“ und %ib2 und %ib3 für das „Digit2“. Weil das oberste Bit das Vorzeichen darstellt, ist „3500“ größer als „8112“!! (siehe Abb. 11.1) Sie können das auch durch Verwendung der Typen sint und usind testen. (siehe Abb. 11.2)

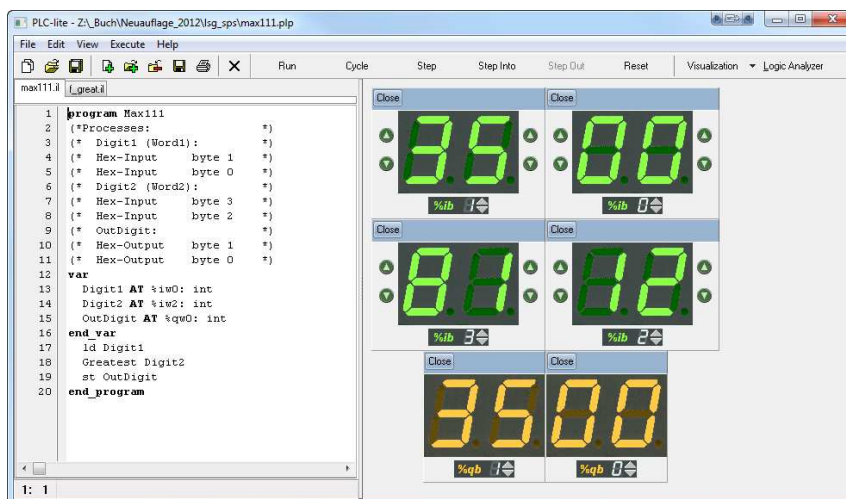


Abb. 11.1 zu Übung 11.5 (MAX111)

```

(* FUNCTION *)
Function Greatest: int
var_input
  D1: int
  D2: int
end_var
ld D1
gt D2
jmpc D1Great

```

```

D2Great:
  ld D2
  st Greatest
  ret
D1Great:
  ld D1
  st Greatest
  ret
end_function

```

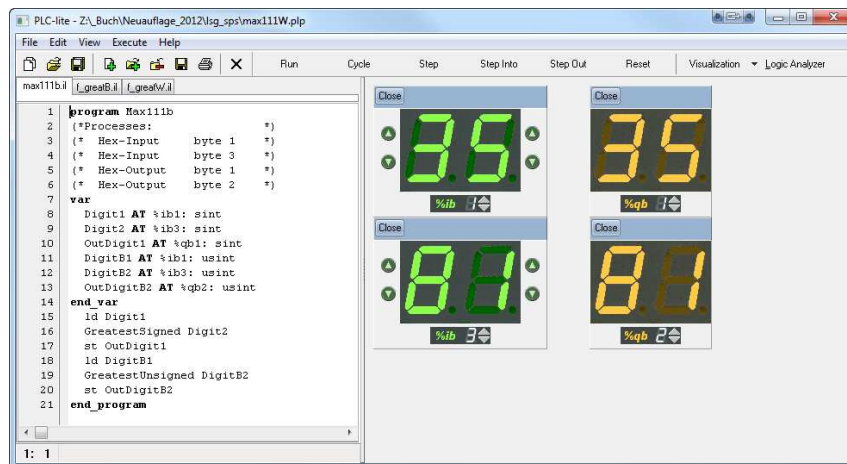


Abb. 11.2 zu Übung 11.5 (MAX111)

```

(* PROGRAM *)
program Max111
(*Processes: *)
(* Digit1 (Word1): *)
(* Hex-Input byte 1 *)
(* Hex-Input byte 0 *)
(* Digit2 (Word2): *)
(* Hex-Input byte 3 *)
(* Hex-Input byte 2 *)
(* OutDigit: *)
(* Hex-Output byte 1 *)
(* Hex-Output byte 0 *)
var
  Digit1 AT %iw0: int
  Digit2 AT %iw2: int

```

```

    OutDigit AT %qw0: int
end_var
    ld Digit1
    Greatest Digit2
    st OutDigit
end_program

```

Übung 11.6 (TIME111)

```

(* FUNCTION *)
FUNCTION_BLOCK SEC01
VAR
    Pulse: TON
END_VAR
VAR_OUTPUT
    Y: Bool
END_VAR
(* Impulsgenerator *)
    ldn Pulse.Q
    st Pulse.IN
    ld t#100ms
    st Pulse.PT
    cal Pulse
    ld Pulse.Q
    st Y
END_FUNCTION_BLOCK

-----

(* PROGRAM *)
program winner
(*Standard-I/O*)
(*%i0.0 reset and start      *)
(*%i0.1 , %i0.2 stopps and  *)
(*shows actual Time1 / Time2*)
(*processes:                  *)
(*      Standard-I/O byte 0 *)
(* act  HEX-Output  byte 1 *)
(* min  HEX-Output  byte 2 *)
(* max  HEX-Output  byte 3 *)
var
    StartReset AT %ix0.0: BOOL
    Stop1 AT %ix0.1: BOOL
    Stop2 AT %ix0.2: BOOL
    Display AT %qb1: Byte
    DisplayMin AT %qb2: Byte

```

```
    DisplayMax AT %qb3: Byte
    Lamp1 AT %qx0.1: BOOL
    Lamp2 AT %qx0.2: BOOL
    c1: ctu
    c2: ctu
    Ticker: sec01
    run1: bool
    run2: bool
end_var
    ld StartReset
    s run1
    s run2
    st c1.r
    st c2.r
    ld Stop1
    r run1
    ld Stop2
    r run2
    ld Ticker.Y
    and run1
    st c1.cu
    ld Ticker.Y
    and run2
    st c2.cu

    cal Ticker
    cal c1
    cal c2

    ld Stop2
    jmpc Display2
    ld Stop1
    jmpc Display1

Display:
    ld c1.cv
    Greatest c2.cv
    int_to_byte
    st Display
MaxDisplay:
    ld c1.cv
    Greatest c2.cv
    int_to_byte
    st DisplayMax
MinDisplay:
```

```

    ld c1.cv
    Least c2.cv
    int_to_byte
    st DisplayMin
    jmp End

Display2:
    ld c2.cv
    int_to_byte
    st Display
    jmp End
Display1:
    ld c1.cv
    int_to_byte
    st Display

End:
    ld run1
    or Stop1
    st Lamp1
    ld run2
    or Stop2
    st Lamp2

end_program

```

Übung 11.7 (DISKR111)

```

(* FUNCTION *)
Function Between: bool
var_input
    z1: sint
    z2: sint
    z3: sint
end_var
    ld z2
    ge z3
    jmpc z32
    ld z2
    lt z3
    jmpc z23
    jmp NotBetween
z23:
    ld z1
    lt z2

```

```

    jmpc NotBetween
    ld z1
    gt z3
    jmpc NotBetween
    jmp IsBetween
z32:
    ld z1
    lt z3
    jmpc NotBetween
    ld z1
    gt z2
    jmpc NotBetween
    jmp IsBetween
NotBetween:
    ld 0
    st Between
    ret
IsBetween:
    ld 1
    st Between
    ret
end_function

```

```

(* PROGRAM *)
program Diskriminator
(*      Standard-I/O byte 0 *)
(*      HEX-Input   byte 0 *)
(* min  HEX-Input   byte 1 *)
(* max  HEX-Input   byte 2 *)
var
    CompValue AT %ib0: sint
    MinValue  AT %ib1: sint
    MaxValue  AT %ib2: sint
    OKLamp    AT %qx0.0: BOOL
end_var
    ld Compvalue
    Between MinValue, MaxValue
    st OKLamp
end_program

```


Kapitel 12

Ablaufsteuerungen

Übung 12.1 (PUSH121)

```
Program PushButton1
(*Processes:                               *)
(* Standard-I/O byte 0                     *)
VAR
  Button AT %ix0.0: BOOL
  Lamp   AT %qx0.0: BOOL
  Step1: bool
  Step2: bool
  Cycle1:bool
END_VAR
  ldn Cycle1
  s   Cycle1
  s   Step1

(* Step 1 *)
  LD   Step1   (*Step 1 activ?   *)
  AND  Button  (*Button pushed?  *)
  R    Step1   (*Step 1 leave   *)
  S    Step2   (*Step 2 activate *)
(* Step 2 *)
  LD   Step2   (*Step 2 activ?   *)
  ANDN Button  (*Button released? *)
  R    Step2   (*Step 2 leave   *)
  S    Step1   (*Step 1 activate *)
(* ACTION *)
  LD   Step2   (*Step 2 activ?   *)
  ST   Lamp    (*Lamp on         *)
end_program
```

Übung 12.2 (PUSH122)

```

Program PushButton2
(*Processes:                               *)
(* Standard-I/O byte 0                     *)
(* Standard-I/O byte 1                     *)
VAR
  Step1 AT %qx1.0: bool
  Step2 AT %qx1.1: bool
  Step3 AT %qx1.2: bool
  Step4 AT %qx1.3: bool
  Cycle1:bool
  Button AT %IX0.0: bool
  Lamp   AT %QX0.0: bool
END_VAR

  ldn Cycle1
  s   Cycle1
  s   Step1
(* Step 1 *)
  LD   Step1   (* Step 1 aktiv?      *)
  AND  Button  (* Button pressed?   *)
  R    Step1   (* Step 1 verlassen *)
  S    Step2   (* Step 2 aktivieren *)
(* Step 2 *)
  LD   Step2   (* Step 2 aktiv?      *)
  ANDN Button  (* Button released?  *)
  R    Step2   (* Step 2 verlassen *)
  S    Step3   (* Step 3 aktivieren *)
(* Step 3 *)
  LD   Step3   (* Step 3 aktiv?      *)
  AND  Button  (* Button pressed?   *)
  R    Step3   (* Step 3 verlassen *)
  S    Step4   (* Step 4 aktivieren *)
(* Step 4 *)
  LD   Step4   (* Step 4 aktiv?      *)
  ANDN Button  (* Button released?  *)
  R    Step4   (* Step 4 verlassen *)
  S    Step1   (* Step 1 aktivieren *)
(* ACTION *)
  LD   Step2   (* Step 2 aktiv?      *)
  OR   Step3   (* Step 3 aktiv?      *)
  ST   Lamp    (* Lamp on            *)
end_program

```

Übung 12.3 (PUSH123)

```

Program PushButton3
(*Processes:                               *)
(* Standard-I/O byte 0                     *)
(* Standard-I/O byte 1                     *)
VAR
  Step1 AT %qx1.0: bool
  Step2 AT %qx1.1: bool
  Step3 AT %qx1.2: bool
  Step4 AT %qx1.3: bool
  Cycle1:bool
  Button AT %IX0.0: bool
  Lamp   AT %QX0.0: bool
END_VAR
  ldn Cycle1
  s   Cycle1
  s   Step1
(* Ablauf der Schrittkette *)
(* Step 1 *)
  LD   Step1
  AND  Button (* Button pressed? *)
  R    Step1
  S    Step2
(* Step 2 *)
  LD   Step2
  ANDN Button (* Button released? *)
  R    Step2
  S    Step3
(* Step 3 *)
  LD   Step3
  AND  Button (* Button pressed? *)
  R    Step3
  S    Step4
(* Step 4 *)
  LD   Step4
  ANDN Button (* Button released? *)
  R    Step4
  S    Step1
(* ACTION *)
  LD   Step2 (* Step 2 activ *)
  S    Lamp (* Lamp on *)
  LD   Step4 (* Step 4 activ? *)
  R    Lamp (* Lamp off *)
end_program

```

Übung 12.4 (TANK121)

```

Program Tank121
(*Processes:                               *)
(* Standard-I/O byte 0                     *)
(* Standard-I/O byte 1                     *)
VAR
  V1 AT %qx0.1: BOOL
  V3 AT %qx0.3: BOOL
  LIS1 AT %ix0.1: BOOL
  LIS2 AT %ix0.2: BOOL
  Start AT %ix0.7: BOOL
  S01 AT %qx1.0:bool
  S02 AT %qx1.1:bool
  S03 AT %qx1.2:bool
  Cycle1:bool
END_VAR
  ldn Cycle1
  s  Cycle1
  s  S03
(* Ablauf der Schrittkette *)
(* STEP 1 *)
  LD  S01  (*Step 1 activ?  *)
  AND LIS2 (*full?        *)
  R   S01  (*Step 1 leave   *)
  S   S02  (*Step 2 activate *)
(* STEP 2 *)
  LD  S02  (*Step 2 activ?  *)
  ANDN LIS1 (*empty?       *)
  R   S02  (*Step 2 leave   *)
  S   S03  (*Step 3 activate *)
(* STEP 3 *)
  LD  S03  (*Step 3 activ?  *)
  AND Start (*Start pushed? *)
  R   S03  (*Step 3 leave   *)
  S   S01  (*Step 1 activate *)
(* ACTION *)
  LD  S01  (*Step 1 activ?  *)
  ST  V1  (*V1 open        *)
  LD  S02  (*Step 2 activ?  *)
  ST  V3  (*V3 open        *)
end_program

```

Übung 12.5 (TANK122)

```

Program Tank122

```

```

(*Processes:                               *)
(* Standard-I/O byte 0                     *)
(* Standard-I/O byte 1                     *)
VAR
  V1 AT %qx0.1: BOOL
  V3 AT %qx0.3: BOOL
  LIS1 AT %ix0.1: BOOL
  LIS2 AT %ix0.2: BOOL
  Start AT %ix0.7: BOOL
  S01 AT %qx1.0:bool
  S02 AT %qx1.1:bool
  S03 AT %qx1.2:bool
  S04 AT %qx1.3:bool
  Cycle1:bool
END_VAR
  ldn Cycle1
  s   Cycle1
  s   S03
(* Ablauf der Schrittkette *)
(* STEP 1 *)
  LD  S01  (*Step 1 activ?  *)
  AND LIS2 (*full?         *)
  R   S01  (*Step 1 leave  *)
  S   S02  (*Step 2 activate *)
(* STEP 2 *)
  LD  S02  (*Step 2 activ?  *)
  ANDN LIS1 (*empty?       *)
  R   S02  (*Step 2 leave  *)
  S   S03  (*Step 3 activate *)
(* STEP 3 *)
  LD  S03  (*Step 3 activ?  *)
  ANDN Start (*Start released?*)
  R   S03  (*Step 3 leave  *)
  S   S04  (*Step 4 activate *)
(* STEP 4 *)
  LD  S04  (*Step 4 activ?  *)
  AND  Start (*Start pressed *)
  R   S04  (*Step 4 leave  *)
  S   S01  (*Step 1 activate *)
(* ACTION *)
  LD  S01  (*Step 1 activ?  *)
  ST  V1  (*V1 open        *)
  LD  S02  (*Step 2 activ?  *)
  ST  V3  (*V3 open        *)
end_program

```

Übung 12.6 (MIXER121)

```

Program TankAndMixer121
(*Processes:                *)
(* Chemical Process (small)*)
VAR
  V1 AT %qx0.1: BOOL
  V3 AT %qx0.3: BOOL
  LIS1 AT %ix0.1: BOOL
  LIS2 AT %ix0.2: BOOL
  Start AT %ix0.7: BOOL
  Stop AT %ix0.6: BOOL
  Lamp AT %qx0.0: BOOL
  Mixer AT %qx0.6: BOOL
  Heater AT %qx0.5: BOOL
  TIC50 AT %ix0.5: BOOL
  V2 AT %qx0.2: BOOL
  V4 AT %qx0.4: BOOL
  LIS3 AT %ix0.3: BOOL
  S01:bool
  S02:bool
  S03:bool
  S04:bool
  S05:bool
  S06:bool
  S06a:bool
  Cycle1:bool
END_VAR
  ldn Cycle1
  s Cycle1
  s S06a
(* STEP 1 *)
  LD S01
  AND LIS2 (*full? *)
  R S01
  S S02
(* STEP 2 *)
  LD S02
  ANDN LIS1 (*empty? *)
  R S02
  S S03
(* STEP 3 *)
  LD S03
  AND TIC50 (*Temp. OK? *)
  R S03
  S S04

```

```

(* STEP 4 *)
LD S04
AND Start (*Start pressed? *)
R S04
S S05
(* STEP 5 *)
LD S05
ANDN LIS3 (*empty? *)
R S05
S S06
(* STEP 6 *)
LD S06
ANDN Start (*Start released?*)
R S06
S S06a
(* STEP 6a *)
LD S06a
AND Start (*Start pressed? *)
R S06a
S S01
(* ACTION *)
LD S01 (*Step 1 activ? *)
ST V1
LD S02 (*Step 2 activ? *)
ST V3
LD S03 (*Step 3 activ? *)
ST Heater
S Mixer
S V2
LD S05 (*Step 5 activ? *)
ST V4
R Mixer
LD S06 (*Step 6 activ? *)
R V2
end_program

```

Übung 12.7 (MIXER122)

```

Program TankAndMixer122
(*Processes: *)
(* Chemical Process (small)*)
VAR
V1 AT %qx0.1: BOOL
V3 AT %qx0.3: BOOL
LIS1 AT %ix0.1: BOOL

```

```

LIS2 AT %ix0.2: BOOL
Start AT %ix0.7: BOOL
Mixer AT %qx0.6: BOOL
Heater AT %qx0.5: BOOL
TIC50 AT %ix0.5: BOOL
V2     AT %qx0.2: BOOL
V4     AT %qx0.4: BOOL
LIS3   AT %ix0.3: BOOL
S01:bool
S02:bool
S03:bool
S04:bool
S05:bool
S06:bool
S06a:bool
Cycle1:bool
TimeMix: TON
END_VAR
  ldn Cycle1
  s   Cycle1
  s   S06a
(* STEP 1 *)
LD   S01
AND  LIS2 (*full?          *)
R    S01
S    S02
(* STEP 2 *)
LD   S02
ANDN LIS1 (*empty?        *)
R    S02
S    S03
(* STEP 3 *)
LD   S03
AND  TIC50 (*Temp. OK? *)
R    S03
S    S04
(* STEP 4 *)
LD   S04
AND  TimeMix.Q (*Time finished? *)
R    S04
S    S05
(* STEP 5 *)
LD   S05
ANDN LIS3 (*empty?          *)
R    S05

```



```
S      S06
(* STEP 6 *)
LD     S06
ANDN   Start (*Start released?*)
R      S06
S      S06a
(* STEP 6a *)
LD     S06a
AND    Start (*Start pressed? *)
R      S06a
S      S01
(* ACTION *)
LD     S01  (*Step 1 activ? *)
ST     V1
LD     S02  (*Step 2 activ? *)
ST     V3
LD     S03  (*Step 3 activ? *)
ST     Heater
S      Mixer
S      V2
LD     S04  (*Step 4 activ? *)
ST     TimeMix.IN
CAL    TimeMix
LD     S05  (*Step 5 activ? *)
ST     V4
R      Mixer
LD     S06a (*Step 6a activ? *)
R      V2
(* Timer *)
LD     t#10s
ST     TimeMix.PT
end_program
```


Kapitel 13

Wiederholungsaufgaben

Übung 13.1 (LOGIK27)

Siehe Abb. 13.1 und 13.2

◇

 


Abb. 13.1 Schaltglieder zu Übung 13.1

a	b	Y	Y1	Y2	Y3	Y4
0	0	1	1	0	1	1
1	0	0	0	0	0	1
0	1	0	1	1	0	1
1	1	0	1	0	0	0

Abb. 13.2 Funktionstabelle zu Übung 13.1

 


Abb. 13.3 Schaltglied zu Übung 13.2

Übung 13.2 (LOGIK28)

Siehe Abb. 13.3

◇

 


Abb. 13.4 Funktion 1 zu Übung 13.3

 


Abb. 13.5 Funktion 2 zu Übung 13.3

 


Abb. 13.6 Funktion 3 zu Übung 13.3

Übung 13.3 (LOGIK29)

Siehe Abb. 13.4 bis Abb. 13.7

◇

Übung 13.4 (LOGIK30)

Siehe Abb. 13.8

◇

Übung 13.5 (FLASH23)

Siehe Abb. 13.9

◇

 


Abb. 13.7 Funktion 4 zu Übung 13.3

a	b	c	d	e	X1	X2	X
1	0	0	0	0	0	1	0
1	1	0	0	0	1	1	1
1	0	1	0	0	1	1	1
1	1	1	0	0	1	1	1
1	0	0	1	0	0	1	0
1	1	0	1	0	1	1	1
1	0	1	1	0	1	1	1
1	1	1	1	0	1	1	1
1	0	0	0	1	0	1	0
1	1	0	0	1	1	1	1
1	0	1	0	1	1	1	1
1	1	1	0	1	1	1	1
1	0	0	1	1	0	0	0
1	1	0	1	1	1	0	0
1	0	1	1	1	1	0	0
1	1	1	1	1	1	0	0

Abb. 13.8 Schaltung zu Übung 13.4

$$X = a \wedge (b \vee c) \wedge (\bar{d} \vee \bar{e})$$

 


Abb. 13.9 Schaltung zu Übung 13.5 (FLASH23)

Übung 13.6 (TEMP51)

```

PROGRAM Temp51
(*Processes:
(* Boiler
VAR
Sw1 AT %IX0.0: BOOL
TIC AT %IX0.4: BOOL
Heat AT %QX0.5: BOOL
Horn AT %QX0.7: BOOL
    
```

```

END_VAR
  LD   Sw1
  ST   Heat
  LDN  TIC
  ST   Horn
END_PROGRAM

```

◇

Übung 13.7 (LOGIK51)

```

Program Logik51
(*Processes:                               *)
(* Standard I/O byte0                       *)
var
  Form      AT %ix0.0: bool
  Druck     AT %ix0.1: bool
  Gitter    AT %ix0.2: bool
  Temp      AT %ix0.3: bool
  Stempel   AT %qx0.0: bool
end_var
  ld   Form
  andn Druck
  and  Gitter
  andn Temp
  st   Stempel
end_program

```

◇

Übung 13.8 (LOGIK52)

```

Program Logik52
(*Processes:                               *)
(* Standard I/O byte0                       *)
var
  Drehzahl AT %ix0.0: bool
  Temp     AT %ix0.1: bool
  Kuehl    AT %ix0.2: bool
  Zulauf   AT %qx0.0: bool
end_var
  ld  Drehzahl
  or  Temp
  or  Kuehl
  stn Zulauf
end_program

```

◇

Übung 13.9 (BOILER53b)

Keine Musterlösung. ◇

Übung 13.10 (BOILER55)

```

Program Boiler55
(*Processes:                *)
(* Standard I/O byte0      *)
var
  PressureOK      AT %ix0.0: bool
  TemperatureOK   AT %ix0.1: bool
  ConcentrationOK AT %ix0.2: bool
  Valve           AT %qx0.0: bool
end_var
  ldn PressureOK
  orn TemperatureOK
  or  ConcentrationOK
  st  Valve
end_program

```

◇

Übung 13.11 (TANK66)

```

Program Tank66
(*Processes:                *)
(* Tanks (small)           *)
VAR
  V1FF : RS
  V3FF : RS
  Start AT %ix0.7: BOOL
  Stop  AT %ix0.6: BOOL
  LIS1  AT %ix0.1: BOOL
  LIS2  AT %ix0.2: BOOL
  V1     AT %qx0.1: BOOL
  V3     AT %qx0.3: BOOL
  Lamp  AT %qx0.0: BOOL
  Run   : BOOL
END_VAR
  ld  Start
  S   Run
  ld  Stop
  R   Run

  ld  Run
  andn V3FF.Q1
  st  V1FF.S

```

```

ld LIS2
st V1FF.R1

ld LIS2
andn V1FF.Q1
st V3FF.S
ldn LIS1
st V3FF.R1

cal V1FF
cal V3FF

ld V1FF.Q1
st V1

ld V3FF.Q1
st V3

ld Run
st Lamp
END_PROGRAM

```

◇

Übung 13.12 (COOLER61)

Keine Musterlösung.

◇

Übung 13.13 (SORTER61)

Keine Musterlösung.

◇

Übung 13.14 (FLASH74)

Keine Musterlösung.

◇

Übung 13.15 (COUNT85)

```

PROGRAM Count85
(*Processes: *)
(* Standard-I/O byte 0 *)
(* Hex-Output byte 1 *)
VAR
Counter : CTD
Disk AT %IX0.2: Bool
ChangeBox AT %QX0.2: Bool
Start AT %IX0.1: Bool
CountValue AT %QB1: INT
END_VAR

```



```

LD 10
ST Counter.PV
LD Disk
ST Counter.CD
LD Start
AND ChangeBox
ST Counter.LD

CAL Counter

LD Counter.Q
ST ChangeBox
LD Counter.CV
ST CountValue
END_PROGRAM

```

◇

Übung 13.16 (COUNT85b)

```

PROGRAM Count85b
(*Processes: *)
(* Standard-I/O byte 0 *)
(* Hex-Output byte 1 *)
(* Hex-Input byte 1 *)
VAR
Counter : CTD
Disk AT %IX0.2: Bool
ChangeBox AT %QX0.2: Bool
Start AT %IX0.1: Bool
CountValue AT %QB1: INT
NumberDisks AT %IB1: INT
END_VAR
LD NumberDisks
ST Counter.PV
LD Disk
ST Counter.CD
LD Start
AND ChangeBox
ST Counter.LD
CAL Counter
LD Counter.Q
ST ChangeBox
LD Counter.CV
ST CountValue
END_PROGRAM

```

◇

Übung 13.17 (MIXER82)

```

Program Mixer82
(*Processes: *)
(* Chemical Process(small) *)
VAR
  V1FF : RS
  V3FF : RS
  Start AT %ix0.7: BOOL
  Stop  AT %ix0.6: BOOL
  LIS1  AT %ix0.1: BOOL
  LIS2  AT %ix0.2: BOOL
  V1     AT %qx0.1: BOOL
  V3     AT %qx0.3: BOOL
  Lamp  AT %qx0.0: BOOL
  Mixer AT %qx0.6: BOOL
  Heater AT %qx0.5: BOOL
  TIC50 AT %ix0.5: BOOL
  V4     AT %qx0.4: BOOL
  LIS3   AT %ix0.3: BOOL
  Run : BOOL
  Fill: BOOL
  Process: BOOL
  Counter: CTD
  Impuls: TP
  CountValue AT %QB3: SINT
END_VAR
  ld  3
  st  Counter.PV

  ld  t#5s
  st  Impuls.PT
  cal Impuls

  ld  Start
  and Counter.Q
  andn Run
  S   Run
  S   Fill
  st  Counter.LD

  cal Counter

  ld  Counter.Q

```

```
R    Fill

ld   Fill
andn V3FF.Q1
st   V1FF.S
ld   LIS2
st   V1FF.R1

ld   LIS2
andn V1FF.Q1
st   V3FF.S
ldn  LIS1
st   V3FF.R1
st   Counter.CD

cal  V1FF
cal  V3FF

ld   V1FF.Q1
st   V1

ld   V3FF.Q1
st   V3

ld   Run
andn Fill
s    Process

ld   Process
andn V4
s    Heater

ld   Process
st   Impuls.IN
ld   Impuls.Q
st   Mixer

ld   Process
and  TIC50
r    Heater
s    V4

ldn  LIS3
and  Process
r    run
```

```

r    Process
r    V4

ld   Run
st   Lamp
LD   Counter.CV
int_to_sint
ST   CountValue

END_PROGRAM

```

◇

Übung 13.18 (FFFB94)

```

program FFFB94
(*Processes: *)
(* Standard-I/O byte 0 *)
var
  FF0: FFRS
  FF1: FFSR
  RSet AT %ix0.0: BOOL
  Set  AT %ix0.1: BOOL
  Out0 AT %qx0.0: BOOL
  Out1 AT %qx0.1: BOOL
end_var

LD  Set
ST  FF0.Set
ST  FF1.Set

LD  RSet
ST  FF0.RSet
ST  FF1.RSet

CAL FF0
CAL FF1

LD  FF0.Y
ST  Out0
LD  FF1.Y
ST  Out1

end_program

```

◇

Übung 13.19 (GEN92)

```

Program ImpulseGEN92
(*Processes: *)
(* Standard-I/O byte 0 *)
(* Hex-Output byte 3 *)
(* - OR - *)
(* Panel *)
var
  Display AT %qb3: SINT
  Counter: CTUD
  Pulse: Puls
  Pulse2:Puls
  runUP AT %i0.7: BOOL
  runDN AT %i0.6: BOOL
end_var
(* Zaehler *)
  ld Pulse.Y
  st Counter.CU
  ld Pulse2.Y
  st Counter.CD

  ld runUP
  st Pulse.run
  ld runDN
  st Pulse2.run

  cal Counter
  cal Pulse
  cal Pulse2

  ld Counter.CV
  int_to_sint
  st Display
end_program

```

◇

Übung 13.20 (TANK101)

```

Program Tank101
(*Processes: *)
(* Tanks (small) *)
(* Hex-Input byte 1 *)
var

```

```

SW1    AT %ix0.0: BOOL
Start  AT %ix0.7: BOOL
Stop   AT %ix0.6: BOOL
LIS1   AT %ix0.1: BOOL
LIS2   AT %ix0.2: BOOL
V1     AT %qx0.1: BOOL
V3     AT %qx0.3: BOOL
V1FF   : RS
V3FF   : RS
Display AT %qb3: sint
PresetValue AT %ib1: int
Counter: CTU
run: bool
end_var

LD     Start
s run
ld PresetValue
st Counter.PV

LD run
ANDN Counter.Q
ANDN V3
ANDN LIS2
ST     V1FF.S
LD     LIS2
ST     V1FF.R1
ST     V3FF.S
LDN LIS1
ST     V3FF.R1

cal V1FF
cal V3FF

ld V3FF.Q1
st V3
st Counter.CU
ld V1FF.Q1
st V1

cal Counter

(* Ist-Wertausgabe / Ende?*)
ld Counter.CV
int_to_sint

```

```

    st Display

    ld Counter.Q
    or Stop
    r run

    ld SW1
    st Counter.R
end_program

```

◇

Übung 13.21 (7SEG103)

Keine Musterlösung.

◇

Übung 13.22 (FLASH105)

```

Program Flash105
(*Processes: *)
(* Standard-I/O byte 1 *)
(* Standard-I/O byte 2 *)
var
    Pulse: TON
    Cycle1: bool
    Bit1 AT %QX1.0: bool
    Bit16 AT %QX2.7: bool
    Byte1 AT %Qw1: uint
    GoLeft AT %IX1.0: BOOL
end_var
(* set Bit *)
    ldn Cycle1
    s Cycle1
    s Bit1

(* Pulsgenerator *)
    ldn Pulse.Q
    st Pulse.IN
    ld t#1000ms
    st Pulse.PT
    cal Pulse

(* Go!! *)
    ldn Pulse.Q
    jmpc PulseOK
    ld GoLeft
    jmpcn RunRight
RunLeft:

```

```

    ld Byte1
    eq 32768
    r Bit16
    r Cycle1

    ld Byte1
    mul 2
    st Byte1
    jmp PulseOK
RunRight:
    ld Byte1
    div 2
    st Byte1
    eq 0
    s Bit16
PulseOK:
end_program

```

◇

Übung 13.23 (DICE102)

```

Program ProgDice102
(*Processes: *)
(* Standard-I/O byte 0 *)
(* Hex-Output byte 0 *)
(* Standard-I/O byte 1 *)
(* Hex-Output byte 1 *)
var
    Start0 AT %ix0.0: BOOL
    Start1 AT %ix0.1: BOOL
    OutByte0 AT %qb0: sint
    OutByte1 AT %qb1: sint
    Dice0: Chance16
    Dice1: Chance16
end_var
    ld Start0
    st Dice0.run
    ld Start1
    st Dice1.run

    cal Dice0
    cal Dice1

    ld Dice0.Value
    st OutByte0
    ld Dice1.Value

```



```

    st OutByte1
end_program

```

◇

Übung 13.24 (DICE103)

```

Program ProgDice103
(*Processes:                               *)
(* Standard-I/O   byte 0                   *)
(* Hex-Output     byte 0                   *)
(* Standard-I/O   byte 1                   *)
(* Hex-Output     byte 1                   *)
var
  Start0 AT %ix0.0: BOOL
  Start1 AT %ix0.1: BOOL
  OutByte AT %qb0: byte
  Dice0: Chance16
  Dice1: Chance16
  Dice1Byte: byte
end_var
  ld Start0
  st Dice0.run
  ld Start1
  st Dice1.run

  cal Dice0
  cal Dice1

  ld Dice1.Value
  mul 16
  sint_to_byte
  st Dice1Byte
  ld Dice0.Value
  sint_to_byte
  or Dice1Byte
  st OutByte
end_program

```

◇

Übung 13.25 (7SEG112)

```

Program SevenSegment112
(*Processes:                               *)
(* Standard-I/O   byte 2                   *)
(* Hex-Input      byte 2                   *)

```

```

(* 7-Segment      byte 1      *)
Var
  InByte1  AT %IB2: byte
  OutByte1 AT %QB1: byte
end_var
  ld InByte1
  byte_to_int
  div 16          (*higher*)
  int_to_7seg
  st OutByte1
end_program

```

◇

Übung 13.26 (7SEG113)

```

Program SevenSegment113
(*Processes:                               *)
(* Standard-I/O  byte 2                     *)
(* Hex-Input     byte 2                     *)
(* 7-Segment     byte 0                     *)
(* 7-Segment     byte 1                     *)
Var
  InByte  AT %IB2: byte
  OutByte0 AT %QB0: byte
  OutByte1 AT %QB1: byte
end_var
  ld InByte
  and 2#00001111      (*lower*)
  byte_to_int
  int_to_7seg
  st OutByte0
  ld InByte
  byte_to_int
  div 16              (*higher*)
  int_to_7seg
  st OutByte1
end_program

```

◇

Übung 13.27 (DICE112)

```

Program ProgDice112
(*Standard-I/O      *)
(*Dice   byte 0     *)
(*Dice   byte 1     *)
var

```

```

    Start0 AT %ix0.0: BOOL
    OutDice0 AT %qb0: BYTE
    Dice0: Chance16
    Start1 AT %ix0.1: BOOL
    OutDice1 AT %qb1: BYTE
    Dice1: Chance16
end_var
    ld Start0
    st Dice0.run
    cal Dice0
    ld Dice0.Value
    int_to_dice
    st OutDice0

    ld Start1
    st Dice1.run
    cal Dice1
    ld Dice1.Value
    int_to_dice
    st OutDice1
end_program

```

◇

Übung 13.28 (MIXER123)

```

Program TankAndMixer123
(*Processes: *)
(* Chemical Process (small)*)
VAR
    V1 AT %qx0.1: BOOL
    V3 AT %qx0.3: BOOL
    LIS1 AT %ix0.1: BOOL
    LIS2 AT %ix0.2: BOOL
    Start AT %ix0.7: BOOL
    Mixer AT %qx0.6: BOOL
    Heater AT %qx0.5: BOOL
    TIC50 AT %ix0.5: BOOL
    V2 AT %qx0.2: BOOL
    V4 AT %qx0.4: BOOL
    LIS3 AT %ix0.3: BOOL
    S01:bool
    S02:bool
    S02b:bool
    S03:bool
    S04:bool

```

```

S05:bool
S05b:bool
S06:bool
S06a:bool
Cycle1:bool
TimeMix: TON
TimeV3: TON
TimeV4: TON
END_VAR
  ldn Cycle1
  s  Cycle1
  s  S06a
(* STEP 1 *)
  LD  S01
  AND LIS2 (*full?          *)
  R  S01
  S  S02
(* STEP 2 *)
  LD  S02
  ANDN LIS1 (*empty?        *)
  R  S02
  S  S02b
(* STEP 2b *)
  LD  S02b
  AND TimeV3.Q (*Time finished? *)
  R  S02b
  S  S03
(* STEP 3 *)
  LD  S03
  AND TIC50 (*Temp. OK? *)
  R  S03
  S  S04
(* STEP 4 *)
  LD  S04
  AND TimeMix.Q (*Time finished? *)
  R  S04
  S  S05
(* STEP 5 *)
  LD  S05
  ANDN LIS3 (*empty?          *)
  R  S05
  S  S05b
(* STEP 5b *)
  LD  S05b
  AND TimeV4.Q (*Time finished? *)

```

```

R    S05b
S    S06
(* STEP 6 *)
LD   S06
ANDN Start (*Start released?*)
R    S06
S    S06a
(* STEP 6a *)
LD   S06a
AND  Start (*Start pressed? *)
R    S06a
S    S01
(* ACTION *)
LD   S01  (*Step 1 activ?  *)
ST   V1
LD   S02  (*Step 2 activ?  *)
S    V3   (*----- Set V3 ----*)
LD   S02b (*Step 2b activ? *)
ST   TimeV3.IN
CAL  TimeV3
LD   S03  (*Step 3 activ?  *)
R    V3   (*---- ReSet V3 ----*)
ST   Heater
S    Mixer
S    V2
LD   S04  (*Step 4 activ?  *)
ST   TimeMix.IN
CAL  TimeMix
LD   S05  (*Step 5 activ?  *)
S    V4   (*----- Set V4 ----*)
R    Mixer
LD   S05b (*Step 5b activ?  *)
ST   TimeV4.IN
CAL  TimeV4
R    V2
LD   S06a (*Step 6a activ?  *)
R    V4   (*---- ReSet V3 ----*)
(* Timer *)
LD   t#10s
ST   TimeMix.PT
LD   t#2s
ST   TimeV3.PT
ST   TimeV4.PT
end_program

```

◇

Übung 13.29 (MIXER124)

```

Program TankAndMixer
(*Processes: *)
(* Chemical Process (big) *)
VAR
  V1 AT %qx0.1: BOOL
  V3 AT %qx0.3: BOOL
  LIS1 AT %ix0.1: BOOL
  LIS2 AT %ix0.2: BOOL
  Start AT %ix0.7: BOOL
  Mixer AT %qx0.6: BOOL
  Heater AT %qx0.5: BOOL
  TIC50 AT %ix0.5: BOOL
  V2 AT %qx0.2: BOOL
  V4 AT %qx0.4: BOOL
  LIS3 AT %ix0.3: BOOL
  LIS11 AT %ix1.1: BOOL
  LIS12 AT %ix1.2: BOOL
  V11 AT %qx1.1: BOOL
  V13 AT %qx1.3: BOOL
  LIS21 AT %ix2.1: BOOL
  LIS22 AT %ix2.2: BOOL
  V21 AT %qx2.1: BOOL
  V23 AT %qx2.3: BOOL
  S01:bool
  S02:bool
  S02b:bool
  S101:bool
  S102:bool
  S102b:bool
  S201:bool
  S202:bool
  S202b:bool
  S03:bool
  S04:bool
  S05:bool
  S05b:bool
  S06:bool
  S06a:bool
  Cycle1:bool
  TimeMix: TON
  TimeV3: TON
  TimeV13: TON
  TimeV23: TON
  TimeV4: TON

```

```

END_VAR
  ldn Cycle1
  s  Cycle1
  s  S06a
(* TANK 0 *)
(* STEP 1 *)
  LD  S01
  AND LIS2  (*full?          *)
  R  S01
  S  S02
(* STEP 2 *)
  LD  S02
  ANDN LIS1  (*empty?        *)
  R  S02
  S  S02b
(* STEP 2b *)
  LD  S02b
  AND  TimeV3.Q (*Time finished? *)
  R  S02b
  S  S101
(* TANK 1 *)
(* STEP 101 *)
  LD  S101
  AND LIS12  (*full?          *)
  R  S101
  S  S102
(* STEP 102 *)
  LD  S102
  ANDN LIS11  (*empty?        *)
  R  S102
  S  S102b
(* STEP 102b *)
  LD  S102b
  AND  TimeV13.Q (*Time finished? *)
  R  S102b
  S  S201
(* TANK 2 *)
(* STEP 201 *)
  LD  S201
  AND LIS22  (*full?          *)
  R  S201
  S  S202
(* STEP 202 *)
  LD  S202
  ANDN LIS21  (*empty?        *)

```

```

R    S202
S    S202b
(* STEP 202b *)
LD   S202b
AND  TimeV23.Q (*Time finished? *)
R    S202b
S    S03
(* STEP 3 *)
LD   S03
AND  TIC50 (*Temp. OK? *)
R    S03
S    S04
(* STEP 4 *)
LD   S04
AND  TimeMix.Q (*Time finished? *)
R    S04
S    S05
(* STEP 5 *)
LD   S05
ANDN LIS3 (*empty? *)
R    S05
S    S05b
(* STEP 5b *)
LD   S05b
AND  TimeV4.Q (*Time finished? *)
R    S05b
S    S06
(* STEP 6 *)
LD   S06
ANDN Start (*Start released?*)
R    S06
S    S06a
(* STEP 6a *)
LD   S06a
AND  Start (*Start pressed? *)
R    S06a
S    S01
(* ACTION *)
LD   S01 (*Step 1 activ? *)
ST   V1
LD   S02 (*Step 2 activ? *)
S    V3 (*----- Set V3 ---*)
LD   S02b (*Step 2b activ? *)
ST   TimeV3.IN
CAL  TimeV3

```



```

LD S101 (*Step 101 activ? *)
ST V11
LD S102 (*Step 102 activ? *)
S V13 (*----- Set V13 ----*)
LD S102b (*Step 102b activ? *)
ST TimeV13.IN
CAL TimeV13
LD S201 (*Step 201 activ? *)
ST V21
LD S202 (*Step 202 activ? *)
S V23 (*----- Set V23 ----*)
LD S202b (*Step 202b activ? *)
ST TimeV23.IN
CAL TimeV23

LD S03 (*Step 3 activ? *)
R V3 (*--- ReSet V3 ---*)
R V13 (*--- ReSet V13 ---*)
R V23 (*--- ReSet V23 ---*)
ST Heater
S Mixer
S V2
LD S04 (*Step 4 activ? *)
ST TimeMix.IN
CAL TimeMix
LD S05 (*Step 5 activ? *)
S V4 (*----- Set V4 ----*)
R Mixer
LD S05b (*Step 5b activ? *)
ST TimeV4.IN
CAL TimeV4
R V2
LD S06a (*Step 6a activ? *)
R V4 (*--- ReSet V3 ---*)
(* Timer *)
LD t#10s
ST TimeMix.PT
LD t#2s
ST TimeV3.PT
ST TimeV13.PT
ST TimeV23.PT
ST TimeV4.PT
end_program

```

◇

Sachverzeichnis

Übungsprojekte

Alarmschaltung 15, 18, 19, 39, 41, 52, 77
Generator 51, 56, 66, 75, 83, 91, 122, 127
Lauflicht 51, 55, 83, 130
Messgefäß 19, 22, 42, 49, 64, 86, 113, 126
Mixer 8, 26, 31, 47, 66, 113, 126
Motorsteuerung 16
Würfel 91, 96, 131

A

Ablaufkette 107
Abwärtszähler 61
Adressierung 29
AE 29
Aktion 107
Aktionsbestimmungszeichen
 nichtspeichernd 108
 speichernd 108
Aktuelles Ergebnis 29
Alarmschaltung *siehe* Übungsprojekte
Antivalenz 36
Anweisungsliste 29
ASCII 5
Ausgangsabbild 38
AWL 29

B

Bündelung 4
BCD 97
bedingter Sprung 83
Belegungsliste 29
Binärzahl 4
Bit 59
Bitfolge 59

Boolesche Algebra 12
Byte 59

C

CTD 61
CTU 60
CTUD 61

D

Datenschalter 8
Datentyp 59
de Morgansche Regeln 31
Dekade 4
Dekoder 93, 97
Dezimalsystem 4
Dezimalzähler 63
Disjunktion 8
Diskriminator 104
Druckschalter 108
Dualsystem 4
Dualzahl 4

E

Eingabewert 93
Eingangsabbild 38
Einschaltverzögerung 56
EXOR 10, 36

F

fallende Flanke 21, 60
Flanke 60
Flip-Flop 15
Funktion 93
 zusammengesetzt 8
Funktionsbaustein 75

G

Generator *siehe* Übungsprojekte

H

Heizungssteuerung 33
 HEX *siehe* Hexadezimalsystem
 Hexadezimalsystem 5, 22, 59, 60, 97

I

Integerzahl 59

K

Kippglied *siehe* Flip-Flop
 Klammer 35
 Klemmenplan 29
 Kommentar 35

L

Laufflicht *siehe* Übungsprojekte

M

Meßgefäß *siehe* Übungsprojekte
 Memory
 Merker 35
 Mengenummessung 72
 Merker 35
 Mischer *siehe* Mixer
 Mixer *siehe* Übungsprojekte
 Modifizierer 31
 Motorsteuerung *siehe* Übungsprojekte
 multiplizieren 83

N

NAND 8
 Negation 8, 31
 NOR 8

O

ODER 8, 29
 Datenschalter 8
 OR 8, 29

P

PAA 38
 PAE 38
 Parallelstruktur 85

Parameter 93
 Parameterübergabe 100
 Parameterliste 104
 Peripherieadressierung 38
 PLC-lite
 Bedienung 29
 Einzelschrittmodus 30
 Funktionsbaustein 77
 Installation 29
 Projektverwaltung 76
 POE 76
 Priorität der Eingangssignale 15
 Programm-Organisations-Einheit 76
 Projekt 76
 Prozessabbild 38
 Prozessabbildregister 38

R

Rückgabewert 93
 Rührer *siehe* Mixer
 RS-Kippglied 15

S

Schreibsperre 16
 Schritt 107
 Sedezimalsystem 5
 Selbsthaltung 37
 7-Segment-Anzeige 88
 7-Segment-Dekoder 93
 Sprung 83, 85
 steigende Flanke 21, 60
 Stoppuhr 104

T

Taktflanke 61
 Taktflankensteuerung 21
 Tank *siehe* Meßgefäß
 Timer 83
 Transitionsbedingung 107
 Trigger 21, 60
 triggern 21

U

Übergangsbedingung 107
 unbedingter Sprung 85
 UND 30
 Datenschalter 8

V

Variable 29
 Verzögerungszeit 56
 vorzeichenlose Integerzahl 59

Vorzugslage 15

W

Würfel *siehe* Übungsprojekte

Weiterschaltbedingung 108

Wort 59

Z

Zähler 22, 59–62, 76, 91, 129

Zahlen

BCD 5

binär 4

HEX 5

negativ 59

vorzeichenbehaftet 59

vorzeichenlos 59

Zeitmessung 69

Zuordnungsliste 29

Zweierkomplement 59